

Homework

3


Due 4/26 at 3:00PM on Gradescope

Please write your answers in the boxes provided for Part 2.


You are not required to submit the solutions to Part 1.

Part 1 (Practice Problems):

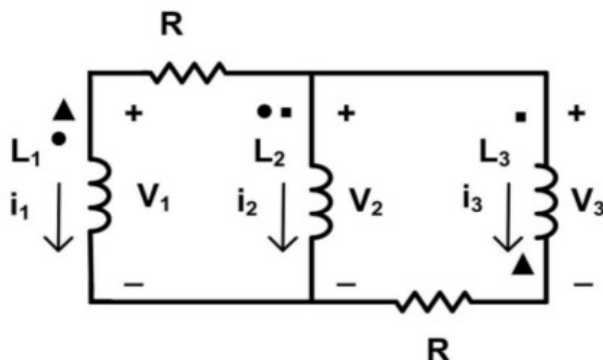- 1) Use the dot convention to find the voltage on the 3 coils in the following circuit. Assume the mutual inductance between any two inductors is M .



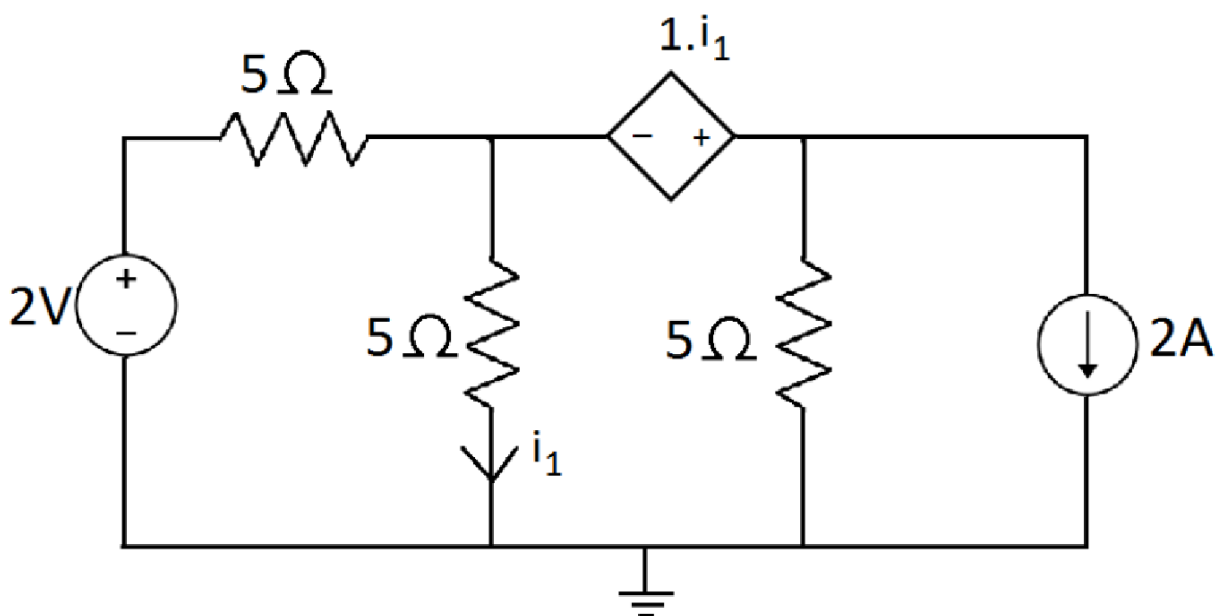
- 2) Use superposition principle to obtain a value for the current i_1 as labeled in the circuit shown below.




Homework

3

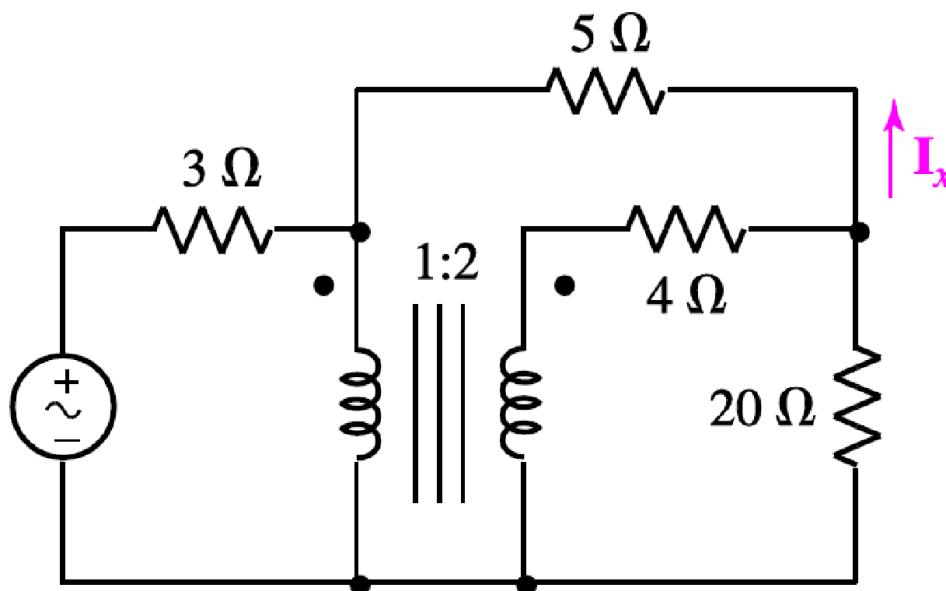3) Find I_x in the circuit below. The transformer is ideal. The voltage source is $100\cos(5t)$.




4) Find the Norton equivalent with respect to the terminals a,b for the circuit shown below.

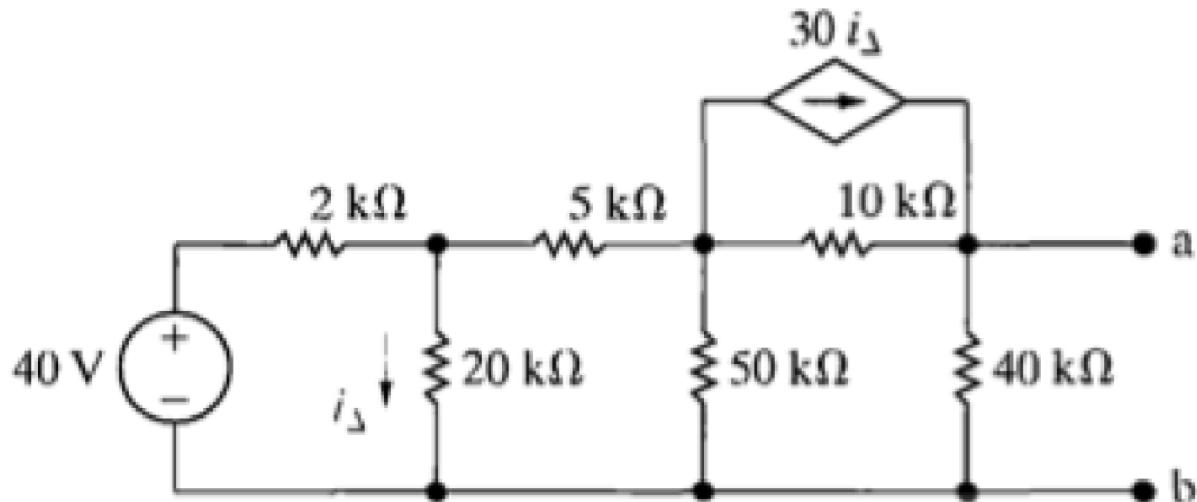

Part 2:

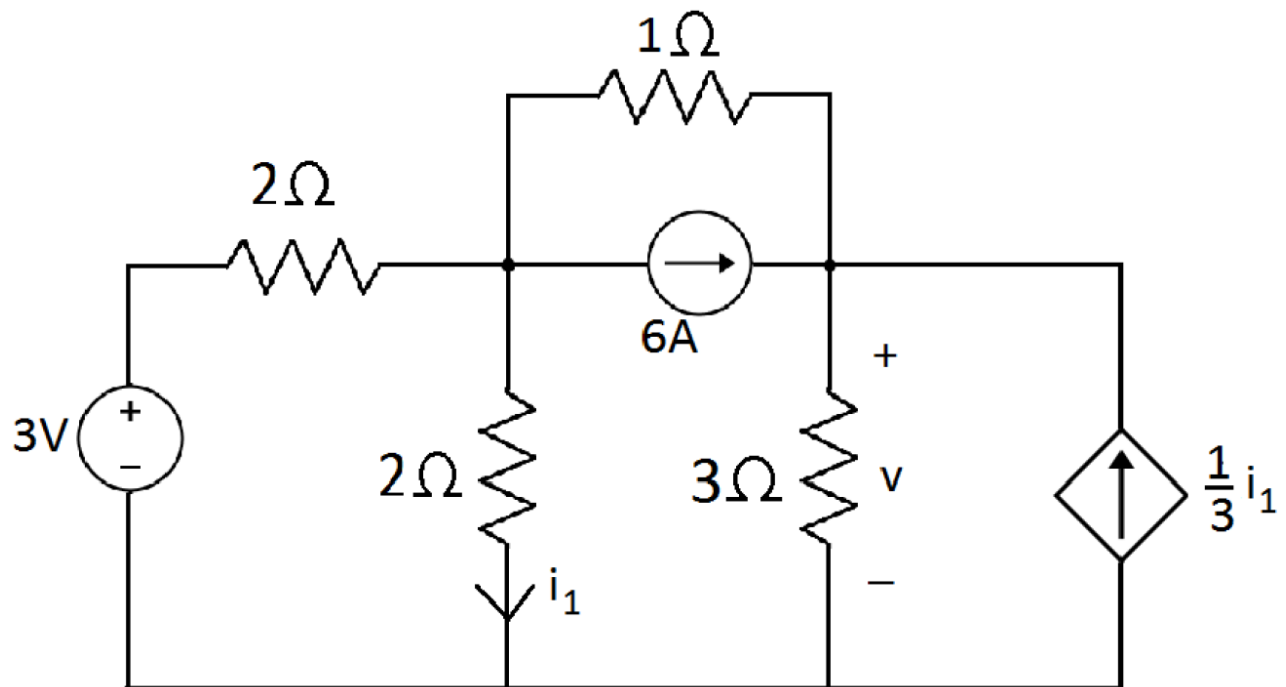
Q1. Use superposition principle in the circuit in the figure below to find the power consumed by that 2Ω resistor which has current i_1 flowing through it (as labeled in the circuit).



$P_{2\Omega} =$

Part 2:

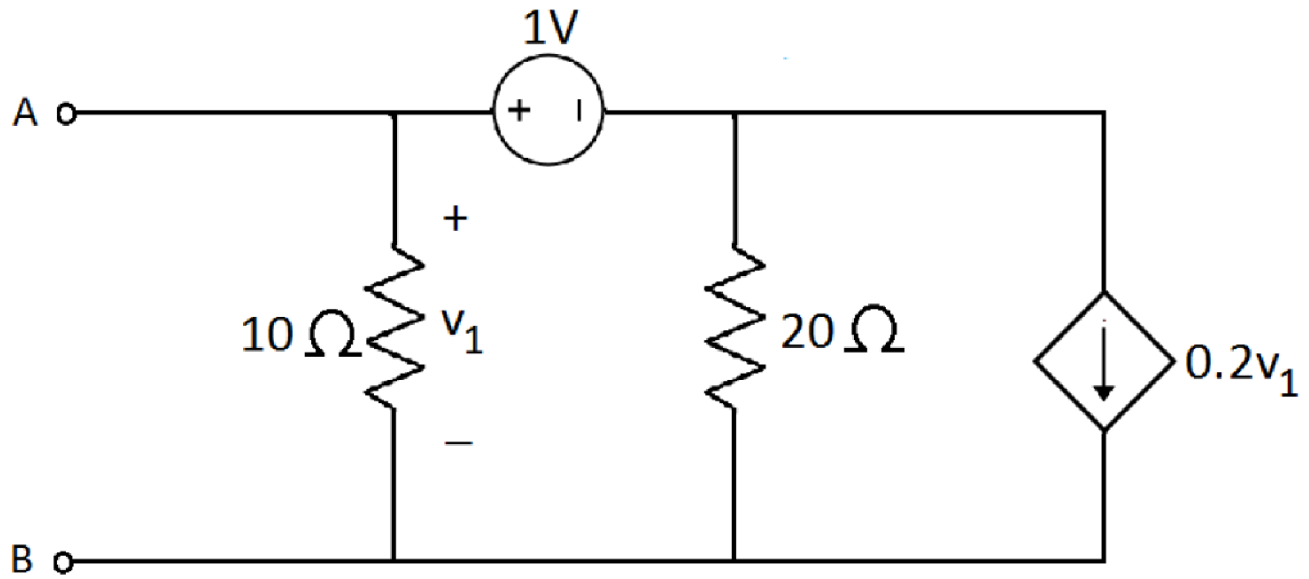Q2. Consider the circuit in the figure below. A resistor R is connected between terminals A and B of the circuit. Find power dissipated in the resistor R when:
 $R=10\Omega$
 $R=20\Omega$




[Hint: Use Norton's theorem to solve this problem.]

$P_R =$

Part 2:

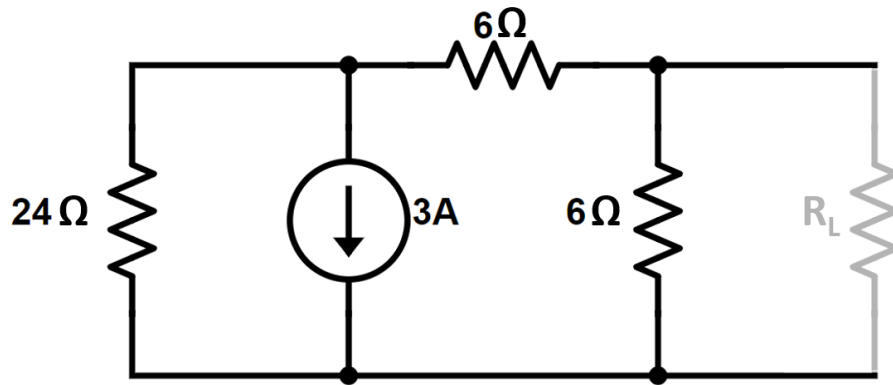Q3. Problem 2.90 from the book. (Copied below)


Find the maximum power that can be delivered to a resistive load by the circuit shown in the figure below. For what value of load resistance (R_L) is the power maximum?



$R_{L,Max} =$

Part 2:

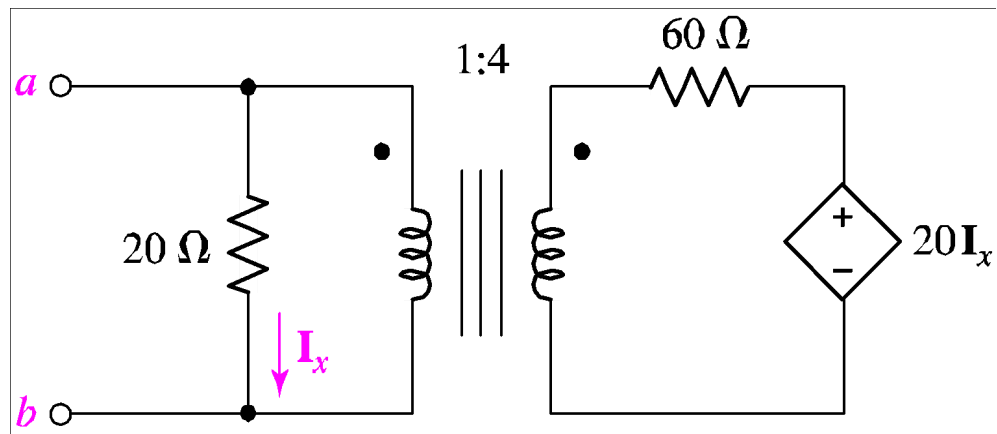Q4. Find the Thévenin equivalent at terminals a and b for the network shown below.



$R_{Th} =$
$V_{Th} =$