
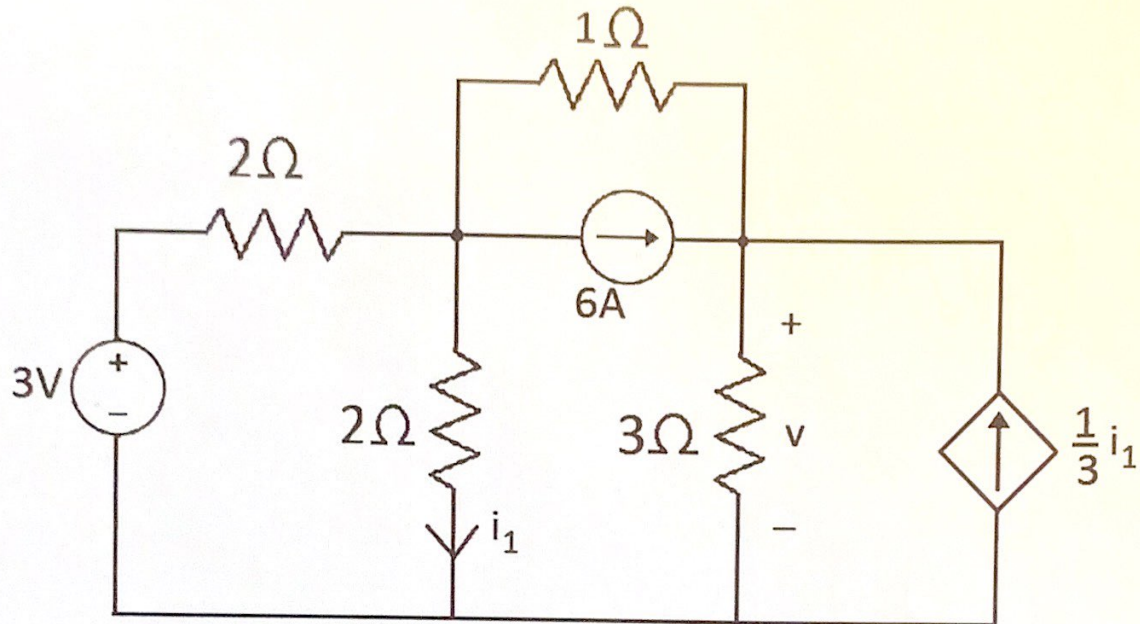


Part 2:

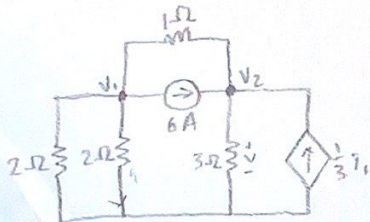Q1. Use superposition principle in the circuit in the figure below to find the power consumed by that 2Ω resistor which has current i_1 flowing through it (as labeled in the circuit).



① Only Current Source Active



Node Voltage Analysis @ V_1

$$\frac{V_1 - 0}{2} + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{1} + 6 = 0$$

Node Voltage Analysis @ V_2


$$\frac{V_2 - V_1}{1} - 6 + \frac{V_2 - 0}{3} - \frac{1}{3} i_1 = 0$$

$$V_1 = -4/3 \quad V_2 = 10/3$$

$$i_1 = \frac{V_1}{2}$$

$$i_1 = -\frac{4}{6} \quad i_1 = -0.67A$$

② Only Voltage Source Active

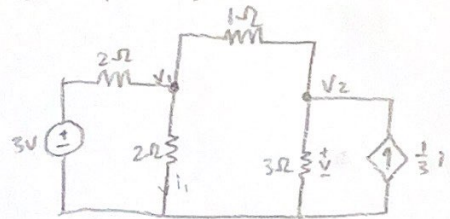

$$\frac{V_1 - 3}{2} + \frac{V_1}{2} + V_1 - V_2 = 0$$

NVA @ V_1

$$\textcircled{1} \frac{V_1 - 3}{2} + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{1} = 0$$

NVA @ V_2

$$\frac{V_2 - V_1}{1} + \frac{V_2 - 0}{3} - \frac{1}{3} i_1 = 0$$

$$\frac{V_2 - V_1}{1} + \frac{V_2}{3} = \frac{1}{3} i_1 \quad (i_1 = \frac{V_1}{2}) \text{ [Ohm's Law]}$$

$$V_2 - V_1 + \frac{V_2}{3} = \frac{1}{3} \left(\frac{V_1}{2} \right)$$

$$V_2 + \frac{V_2}{3} - V_1 - \frac{V_1}{6} = 0$$

$$\textcircled{2} \left(1 + \frac{1}{3} \right) V_2 + \left(-1 - \frac{1}{6} \right) V_1 = 0$$

$$V_1 = \frac{4}{3} V_2 = \frac{7}{6}$$

$$i_1 = 0.67A$$

$$P_{2\Omega} = 0W$$

$$i_1 = 0A? \quad P_{2\Omega} = 0W?$$

eh

Part 2:


Q2. Consider the circuit in the figure below. A resistor R is connected between terminals A and B

of the circuit. Find power dissipated in the resistor R when:

$$R=10\Omega$$

$$R=20\Omega$$

$$V_1 = V_{oc}$$

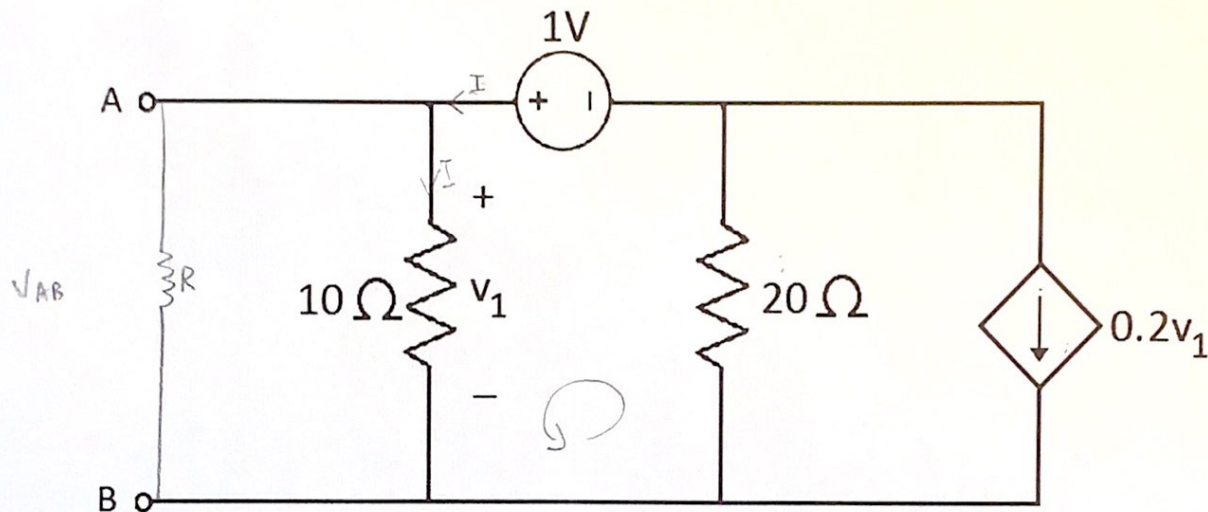

[Hint: Use Norton's theorem to solve this problem.]

Use KVL on middle loop to solve for I

$$1 - V_1 - 20(I + 0.2V_1) = 0$$

$$1 - V_1 - 20I - 4V_1 = 0$$


$$V_1 = 10I$$

$$1 - 10I - 20I - 40I = 0$$

$$-70I = -1$$

$$I = \frac{1}{70} \text{ A} \quad V_1 = \frac{1}{7} \text{ V} = V_{AB}$$


Short Circuit

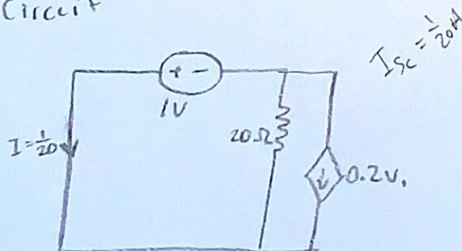

$$R_T = \frac{V_T}{I} = \frac{\frac{1}{7}}{\frac{1}{70}} = 10\Omega$$

Norton Equivalent

$$R = 10\Omega$$

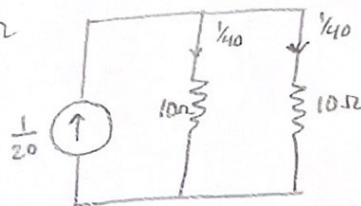


$$P = I^2 R$$

$$P = \left(\frac{1}{40}\right)^2 \times 10 = 0.00625 \text{ W}$$

$$R = 10\Omega \quad P = 0.00625 \text{ W}$$

$$R = 20\Omega$$

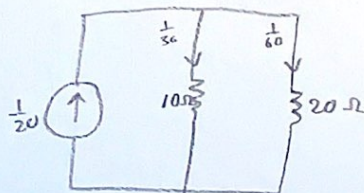

$$P = I^2 R$$

$$P = \left(\frac{1}{60}\right)^2 \times 20 = 0.0055 \text{ W}$$

$$R = 20\Omega$$


$$P = 0.0055 \text{ W}$$

$$P_R = 0.00625 \text{ W}, 0.0055 \text{ W}$$


Part 2:

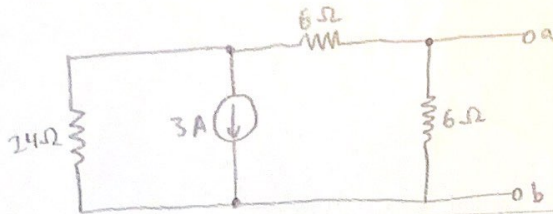Q3. Problem 2.90 from the book.

Find the maximum power that can be delivered to a resistive load by the circuit shown below. For what value of load resistance is the power maximum?



• Find R_T

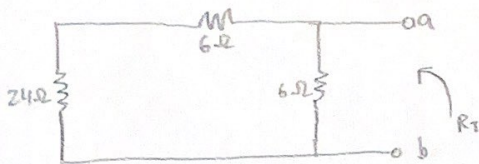

$$\frac{d}{dR_L} P_L = 0$$


$$24 + 6 = 30\Omega$$

$$30 \parallel 6 = \frac{30 \times 6}{30 + 6} = \frac{180}{36} = 5\Omega$$

$$R_T = 5\Omega$$

• Find V_T

Source Transformation

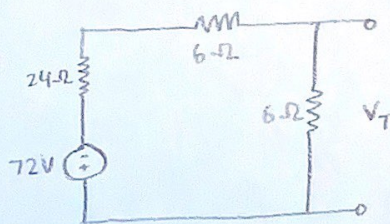

Voltage Division Method

$$V_T = 72 \frac{6}{24 + 6 + 6}$$

$$V_T = -12V$$

$$P = \frac{V_T^2}{4 \cdot R_L}$$

• Maximum Power

$$P_R = \frac{V_T^2}{4R_L}$$


$$P_R = \frac{(-12)^2}{4 \cdot 5} = \frac{144}{20} = 7.2W$$

The maximum power delivered is 7.2W.

For maximum power transfer, $R_L = R_T = 5\Omega$.

$$P_R = 7.2W$$

OK

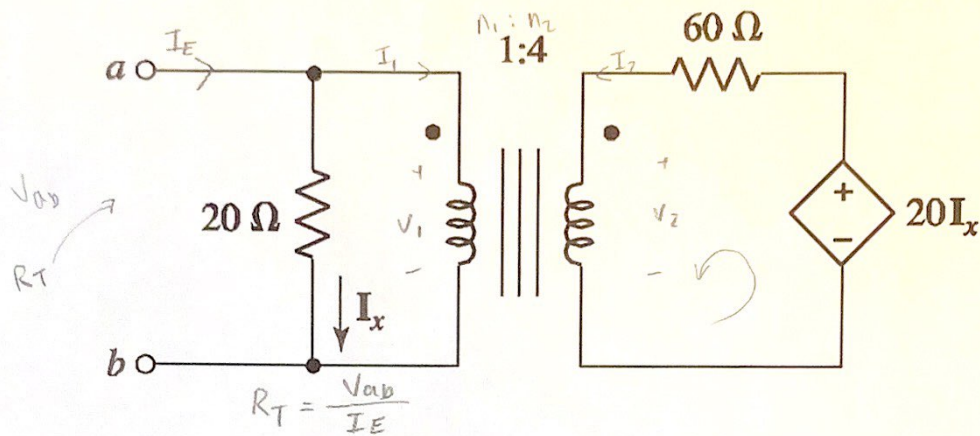Part 2:Q4. Find the Thévenin equivalent at terminals a and b for the network shown below.

$$\begin{cases} V_2 = nV_1 & i_2 = -\frac{1}{n}i_1 \\ \frac{V_1}{V_2} = \frac{n_1}{n_2} & -\frac{i_2}{i_1} = \frac{n_1}{n_2} \end{cases}$$

$$\begin{aligned} \textcircled{1} \quad & I_E = I_x + I_1 \quad (\text{KCL}) \\ \textcircled{2} \quad & I_x = \frac{V_{ab}}{20} \quad (\text{Ohm's Law}) \\ \textcircled{3} \quad & V_2 = 20I_x + 60(-I_2) \quad (\text{KVL}) \end{aligned}$$

$$\frac{V_{ab}}{V_2} = \frac{1}{4} \quad \frac{I_1}{-I_2} = \frac{1}{4}$$

$$\frac{V_{ab}}{V_2} = \frac{1}{4} \quad \frac{-I_2}{I_1} = \frac{1}{4}$$

$$\textcircled{4} \quad V_2 = 4V_{ab} \quad \textcircled{5} \quad I_1 = -4I_2$$

$$4V_{ab} = 20I_x - 60I_2$$

$$4V_{ab} = 20I_x - 60\left(-\frac{I_1}{4}\right)$$

$$4V_{ab} = 20I_x + 15I_1$$

$$4V_{ab} = 20I_x + 15I_1$$

$$4V_{ab} = 20\left(\frac{V_{ab}}{20}\right) + 15I_1$$

$$4V_{ab} = V_{ab} + 15I_1$$

$$3V_{ab} = 15I_1$$

$$V_{ab} = 5I_1$$

$$I_1 = \frac{V_{ab}}{5}$$

$$I_E = \frac{V_{ab}}{20} + \frac{V_{ab}}{5}$$

$$I_E = \frac{1}{4}V_{ab}$$

$$R_T = \frac{V_{ab}}{I_E}$$

$$R_T = \frac{5I_1}{\frac{1}{4}(5I_1)}$$

$$R_T = 4\Omega$$

$$\begin{aligned} V_T &= 0 & V_{oc} \\ I_N &= 0 & I_{sc} \end{aligned}$$

Thévenin: $R_T = 4\Omega$