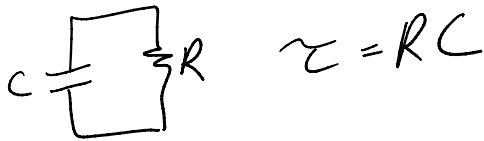


First Order Circuits

Time Constant $\rightarrow \tau$ $e^{-t/\tau}$
 - Settling time for 63% to final value.

"The switch has been closed for a long time."


Capacitor (V cannot change instantly)



$$V_C(t \leq 0) = 10V$$

$$V_C(t \geq 0) = 10e^{-t/RC}$$


Inductor (I cannot change instantly)

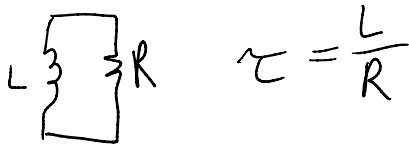

$$I_L(t \leq 0) = 10A$$

$$I_L(t \geq 0) = 10e^{-t/\tau}$$

First Order Circuit Response

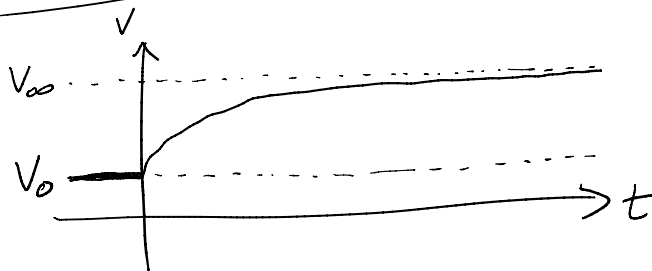


$$V(t \leq 0) = V_0$$

$$V(t \rightarrow \infty) = V_{\infty}$$

$$V(t \geq 0) = V_0 + (V_{\infty} - V_0)(1 - e^{-t/\tau})$$


V for Cap
or
I for Ind

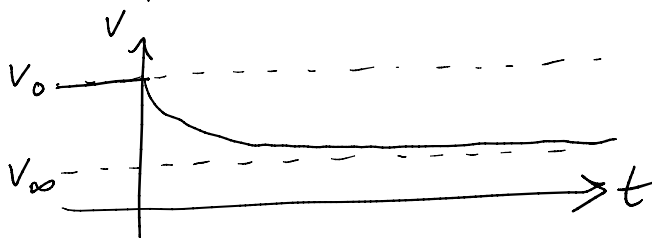

$$V(t \leq 0) = V_0$$

$$V(t \rightarrow \infty) = V_{\infty}$$
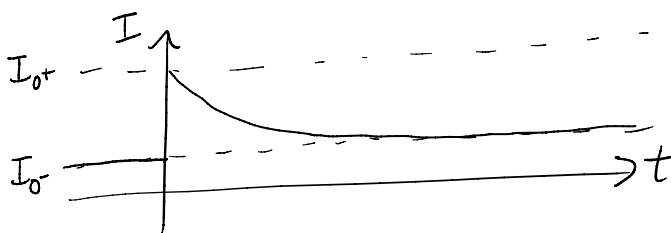
$$V(t \geq 0) = V_{\infty} + (V_0 - V_{\infty})e^{-t/\tau}$$



$$I(t < 0) = I_{0-}$$

$$I(t \rightarrow \infty) = I_{0-}$$


$$I(t > 0) = I_{0-} + (I_{0+} - I_{0-})e^{-t/\tau}$$



$$I(t < 0) = I_{0-}$$


$$I(t \rightarrow \infty) = I_{0+}$$
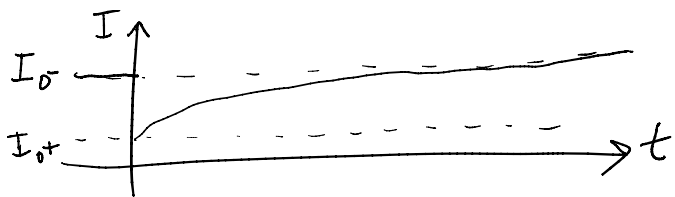
$$I(t > 0) = I_{0+} + (I_{0-} - I_{0+})(1 - e^{-t/\tau})$$



$$I(t \rightarrow \infty) = I_0-$$
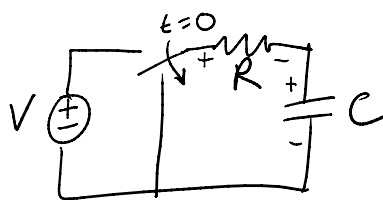
$$I(t > 0) = I_0+ + (I_0- - I_0+)(1 - e^{-t/\tau})$$




$$V_C(t \leq 0) = V$$

$$V_C(t \rightarrow \infty) = 0$$

$$V_C(t \geq 0) = V e^{-t/\tau_{RC}}$$

$$V_R(t > 0) = -V e^{-t/\tau_{RC}}$$

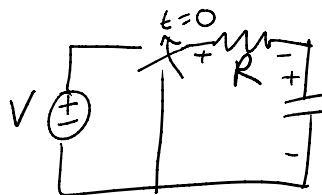

$$V_C(t \leq 0) = 0$$

$$V_C(t \rightarrow \infty) = V$$


$$V_C(t \geq 0) = V(1 - e^{-t/\tau_{RC}})$$

$$V_R(t < 0) = 0$$

$$V_R(t \rightarrow \infty) = 0$$

$$V_R(t > 0) = V - V(1 - e^{-t/\tau_{RC}})$$


$$V_R(t > 0) = V e^{-t/\tau_{RC}}$$

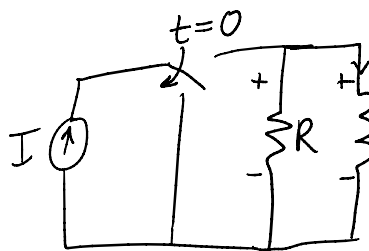

$$I_L(t \leq 0) = I$$

$$I_L(t \rightarrow \infty) = 0$$




$$I_L(t \geq 0) = I e^{-t/\tau_L}$$

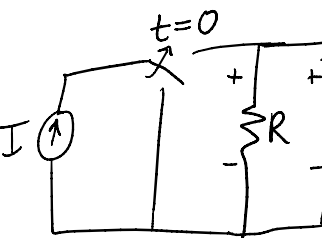

$$I_L(t \leq 0) = 0$$

$$I_L(t \rightarrow \infty) = I$$

$$I_L(t \geq 0) = I(1 - e^{-t/\tau_L})$$

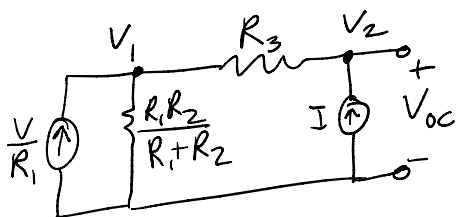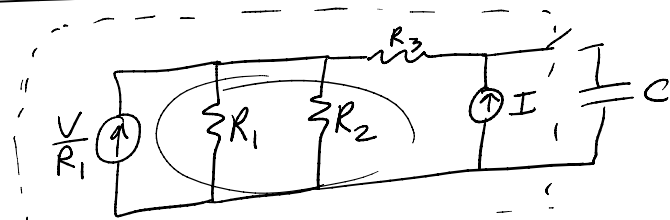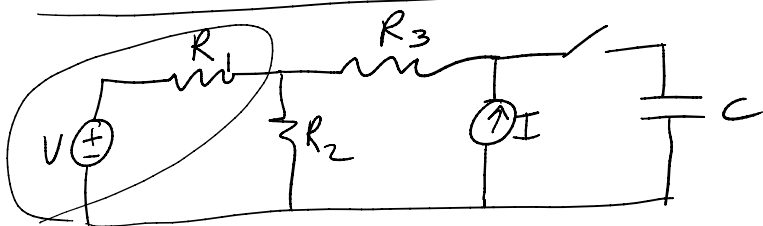


$$\textcircled{1} \frac{V}{R_1} = \frac{V_1(R_1 + R_2)}{R_1 R_2} + \frac{V_1 - V_2}{R_3} = \left(\frac{R_1 + R_2}{R_1 R_2} + \frac{1}{R_3} \right) V_1 - \frac{V_2}{R_3}$$

$$\textcircled{2} I = \frac{V_2 - V_1}{R_3} \Rightarrow V_2 = I R_3 + V_1$$

$$\frac{V}{R_1} = \left(\frac{R_1 + R_2}{R_1 R_2} + \frac{1}{R_3} \right) V_1 - \frac{I R_3 + V_1}{R_3} = \frac{R_1 + R_2}{R_1 R_2} V_1 - I$$

$$\left(\frac{V}{R_1} + I \right) \frac{R_1 R_2}{R_1 + R_2} = V_1$$
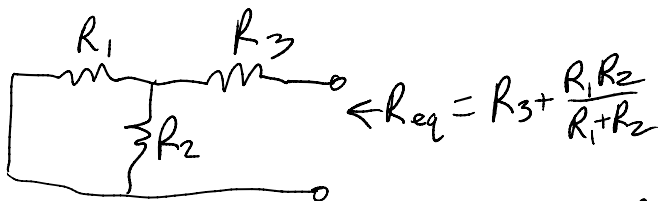
$$V_2 = V_{OC} = V_{Th} = I R_3 + \frac{V R_2}{R_1 + R_2} + \frac{I R_1 R_2}{R_1 + R_2}$$



$$R_{eq} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

$$\tau = \left(R_3 + \frac{R_1 R_2}{R_1 + R_2} \right) C$$



