

## Part 2 (Graded):

### Q1. Problem 11.29

The transistor in the figure below has  $KP = 50 \mu A/V^2$ ,  $W = 600 \mu m$ ,  $L = 20 \mu m$ , and  $V_{t0} = 1V$ . Determine the values of  $R_1$  and  $R_s$ .


Device Constant

$$K = \frac{W}{L} \frac{KP}{2}$$

$$K = \left( \frac{600 \times 10^{-6}}{20 \times 10^{-6}} \right) \frac{50 \times 10^{-6}}{2}$$

$$K = 0.75 \frac{mA}{V^2}$$

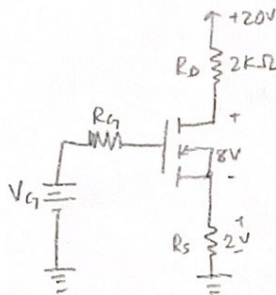Redraw Circuit ( $R_{G1} = R_1 \parallel 1M\Omega$ )



$$V_{G1} = V_{DD} \left[ \frac{10^6}{R_1 + 10^6} \right]$$

$$V_{DD} = I_{DQ} R_D + 8 + 2$$


$$20 = 2000 I_{DQ} + 10$$

$$I_{DQ} = 5mA$$

$$R_s = \frac{V_s}{I_{DQ}} =$$

$$R_s = \frac{2}{5 \times 10^{-3}}$$

$$R_s = 400\Omega$$

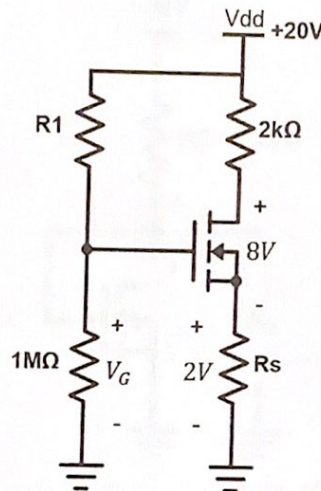

We want to bias the transistor in saturation region.

$$I_{DQ} = K (V_{GSQ} - V_{t0})^2$$

$$5 \times 10^{-3} = 0.75 \times 10^3 (V_{GSQ} - 1)^2$$

$$V_{GSQ}^2 - 2V_{GSQ} - 5.67 = 0$$

$$V_{GSQ} = 3.582V, V_{GSQ} = -1.582V$$

$$\text{For saturation, } V_{GSQ} > V_{t0} : V_{GS} = 3.582V$$

$$V_{G1} = V_{GSQ} + R_s I_{DQ}$$

$$V_{G1} = 3.582 + 400(0.005)$$

$$V_{G1} = 5.582V$$

$$V_{G1} = V_{DD} \left[ \frac{10^6}{R_1 + 10^6} \right]$$

$$5.582 = 20 \left[ \frac{10^6}{R_1 + 10^6} \right]$$

$$R_1 = 2.618 \times 10^6 \Omega$$



$$R_s = 400\Omega$$

$$R_1 = 2.618 \times 10^6 \Omega$$

## Q2. Problem 11.53

Find  $V_{DSQ}$  and  $I_{DQ}$  for the FET shown in the figure below, given  $V_{t0} = 3V$  and  $K = 0.5mA/V^2$ . Find the value of  $g_m$  at the operating point. Draw the small-signal equivalent circuit, assuming that  $r_d = \infty$ . Derive an expression for the resistance  $R_0$  in terms of  $R_D$  and  $g_m$ . Evaluate the expression for the values given.

Small-signal equivalent circuit

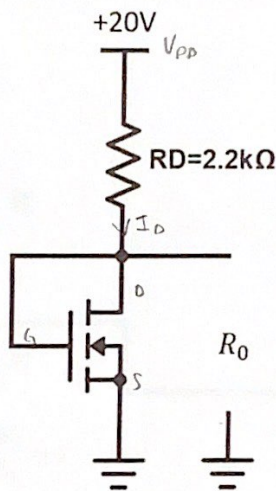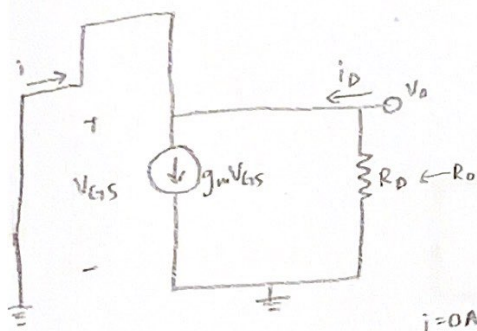

G and S are both shorted,

$$V_{GS} = V_{GS}$$

At quiescent point:

$$V_{DS} = V_{DSQ}, V_{GS} = V_{GSQ}, I_D = I_{DQ}$$

$$V_{DSQ} = V_{GSQ}, V_{DSQ} = V_{GSQ}$$

$$V_{DSQ} = V_{DD} - R_D I_{DQ}$$

$$I_{DQ} = \frac{V_{DD} - V_{DSQ}}{R_D}$$

Saturation:  $V_{DS} \geq V_{GS} - V_{t0}$

• This is true, since  $V_{DS} = V_{GS}$   
 ↳ Transistor in saturation!

$$I_{DQ} = K(V_{GS} - V_{t0})^2$$

$$I_{DQ} = K(V_{DSQ} - 3)^2$$

Combining equations for  $I_{DQ}$ :

$$\frac{V_{DD} - V_{DSQ}}{R_D} = K(V_{DSQ} - 3)^2$$

$$\frac{20 - V_{DSQ}}{2200} = 0.0005(V_{DSQ} - 3)^2$$

$$V_{DSQ} = 6.616V$$

$$V_{DSQ} = -1.5252V$$

(must be positive)

$$I_{DQ} = K(V_{DSQ} - 3)^2$$

$$I_{DQ} = 0.0005(6.616 - 3)^2$$

$$I_{DQ} = 6.54mA$$

$$I_{DQ} = K(V_{DSQ} - V_{t0})^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

$$g_m = 2K(V_{GSQ} - V_{t0})$$

$$g_m = 0.001(6.616 - 3)$$

$$g_m = 3.616 \frac{mA}{V}$$

Looking at equivalent circuit

$$V_o = V_{GS}$$

$$i_D = g_m V_{GS} + \frac{V_o}{R_D}$$

$$R_o = \frac{V_o}{i_D}$$

$$R_o = \frac{V_o}{g_m V_{GS} + \frac{V_o}{R_D}} = \frac{V_{GS}}{g_m V_{GS} + \frac{V_o}{R_D}}$$

$$R_o = \frac{1}{g_m + \frac{1}{R_D}}$$


$$R_o = \frac{1}{3.616 \times 10^{-3} + (2200)^{-1}}$$

$$R_o = 245\Omega$$


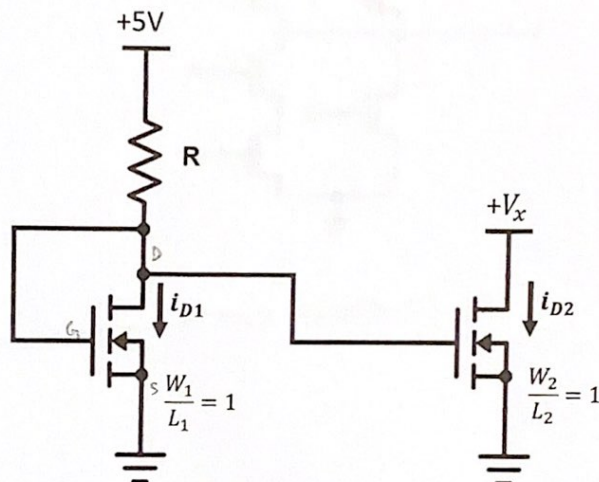
### Q3. Problem 11.35

Both transistors shown in the figure below have  $KP = 100 \mu A/V^2$  and  $V_{t0} = 0.5V$ . Determine the value of  $R$  needed so that  $i_{D1} = 0.2mA$ . For what range of  $V_x$  is the second transistor operating in the saturation region? What is the resulting value of  $i_{D2}$ ? Provided that  $V_x$  is large enough so that the second transistor operates in saturation, to what ideal circuit element is the transistor equivalent?



$V_{G01} = 0V \rightarrow$  Transistor #1 in saturation

$$K_1 = \frac{1}{2} KP \left( \frac{W_1}{L_1} \right)$$

$$K_1 = \frac{1}{2} (100 \times 10^{-6})$$

$$K_1 = 50 \times 10^{-6} A/V^2$$

$$i_{D1} = K_1 (V_{GS1} - V_{t0})^2$$

$$0.2 \times 10^{-3} = 50 \times 10^{-6} (V_{GS1} - 0.5)^2$$

$$V_{GS1} = -1.5V, V_{GS1} = 2.5V$$

In saturation, must be positive

$$V_{GS1} = 2.5V$$

$$R = \frac{V_{DD} - V_{GS1}}{i_{D1}}$$

$$R = \frac{5 - 2.5}{0.2 \times 10^{-3}}$$

$$R = 12,500 \Omega$$

Transistor #2

$$K_2 = \frac{1}{2} KP \left( \frac{W_2}{L_2} \right)$$

$$K_2 = \frac{1}{2} (100 \times 10^{-6})$$

$$K_2 = 50 \times 10^{-6} A/V^2$$

$$i_{D2} = K_2 (V_{GS2} - V_{t0})^2$$


$$i_{D2} = 50 \times 10^{-6} (2.5 - 0.5)^2$$

[ $V_{GS2}$  is same in both transistors because they share the same  $KP$  and  $V_{t0}$ ]

$$i_{D2} = 0.4 mA$$

As long as  $V_x > 2V$ , then transistor #2 will be in saturation. This allows  $i_{D2}$  to be constant at  $0.4mA$ . Thus,  $i_{D2}$  essentially behaves as a  $0.4mA$  current source.

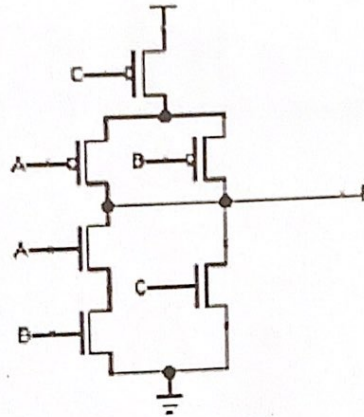Q4. Analyze the CMOS circuit below (triode region equivalent) and fill out the "truth table" for it.



This CMOS circuit is equivalent to the logic equation

$$F = \overline{AB + C}$$

$$F = \overline{(A \wedge B) \vee C}$$

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0