

Homework 2


Due 4/19 at 3:00PM on Gradescope

Please write your answers in the boxes provided for Part 2.


You are not required to submit the solutions to Part 1.

Part 1 (Practice Problems):

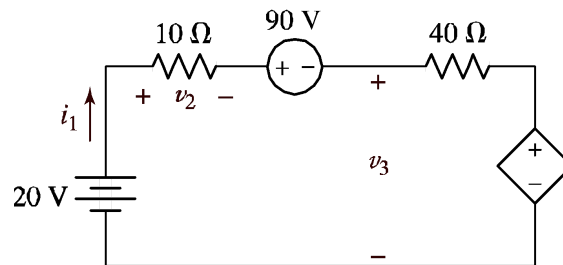
- 1) Refer to the circuit of figure below and label the dependent source αv_3 . Find v_3 and α if (a) the 90 V source generates 180 W; (b) the 90 V source absorbs 180 W.



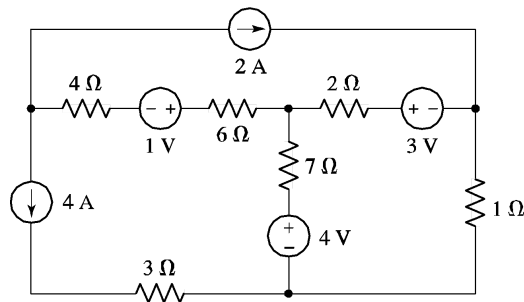- 2) Determine the power supplied by the 2 A source in the circuit below. (Use source transformations)



- 3) Find v_3 in the circuit below if element A is (a) a short circuit; (b) a 9 V independent voltage source, with positive reference on the left.

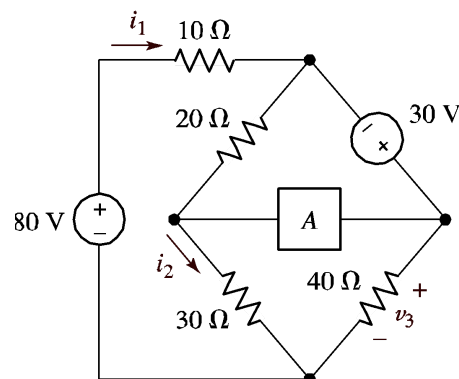

Part 2:

Q1. Fig 1 below shows 2 equivalent circuits (a) and (b). In circuit (a) the 2 coupled inductors have self-inductances L_1 and L_2 as shown and a mutual inductance M . Find L_A , L_B and L_C in terms of L_1 , L_2 and M .

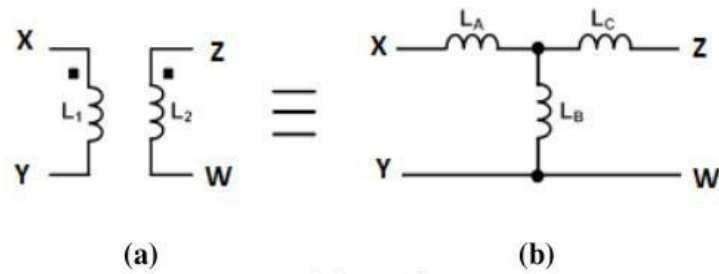


Figure 1

$L_A =$
$L_B =$
$L_C =$

Part 2:

Q2. Use a series of source transformations to find the current i_o in the circuit given in the Fig 2 below.


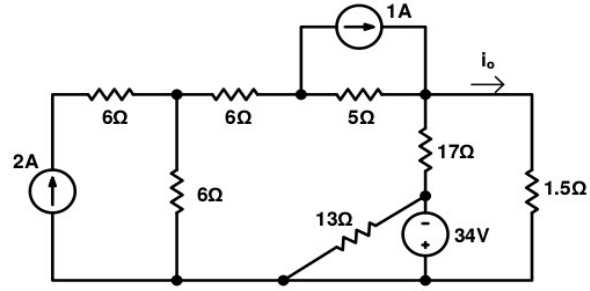


Figure 2

$i_o =$

Part 2:

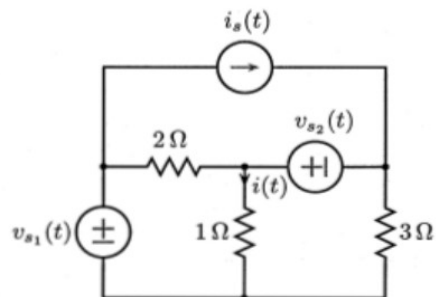
Q3. Refer circuit below. Find $i(t)$ (current flowing through the 1 ohm resistor) in terms of $i_s(t)$, $v_{s1}(t)$, $v_{s2}(t)$.



$i(t) =$

Part 2:

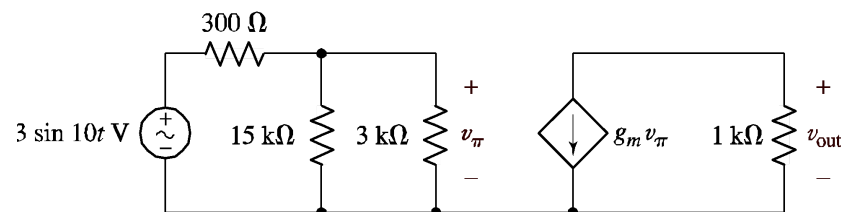Q4. The circuit below is a commonly used equivalent circuit used to model the ac behavior of a bipolar junction transistor amplifier circuit. If $g_m = 38 \text{ mS}$ compute v_{out} .



$v_{\text{out}} =$