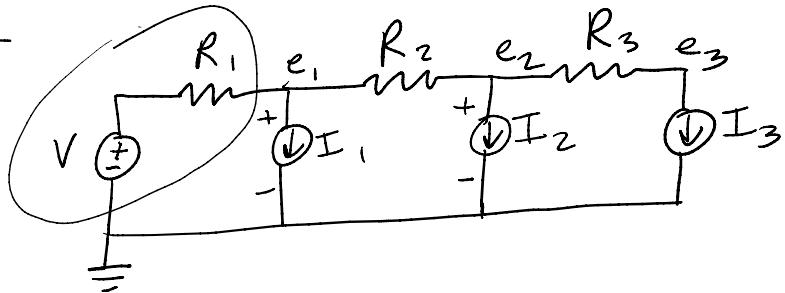


Midterm

$$I_1, I_2, I_3 = I_{\text{out}}$$

↑
On Off

$$G \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = S$$

$$\begin{bmatrix} \frac{V}{R_1} - I_1 \\ I_2 \\ I_3 \end{bmatrix} = S \quad G \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & 0 \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} \\ 0 & -\frac{1}{R_3} & \frac{1}{R_3} \end{bmatrix}$$


All current sources on.

$$P_{\text{Max}} = 3IV$$

Def: $P = VI$



$$V_1 \text{ off: } i_1 = \frac{V_2 + V_3}{R}$$
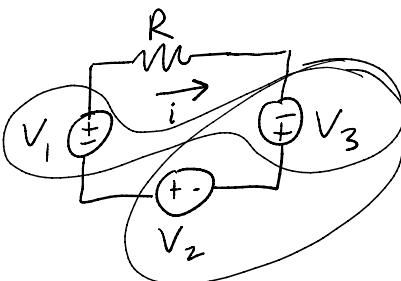
$$V_2 \text{ off: } i_2 = \frac{V_1 + V_3}{R}$$






$$i = \frac{V_1 + V_2 + V_3}{R}$$
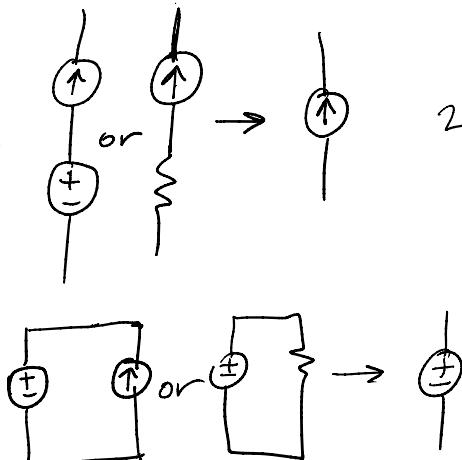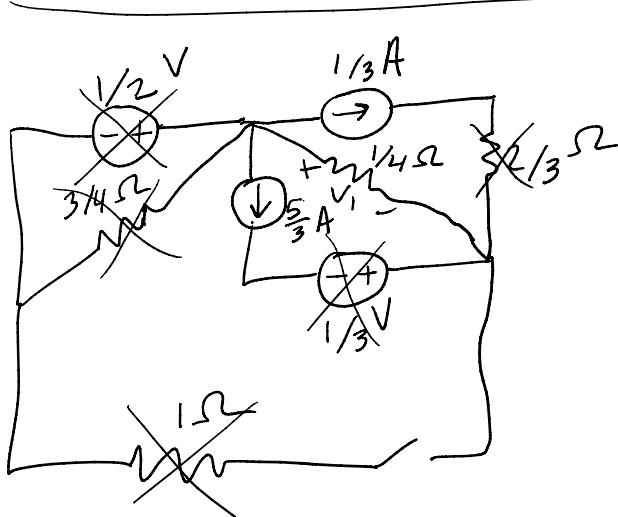
$$i = i_1 + i_2 = \frac{V_1 + V_2 + 2V_3}{R}$$



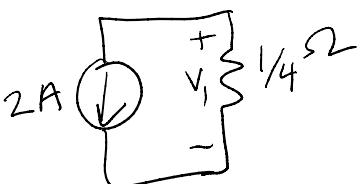
$$V_1 = -2\left(\frac{1}{4}\right) = -\frac{1}{2}$$




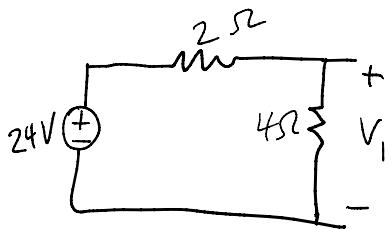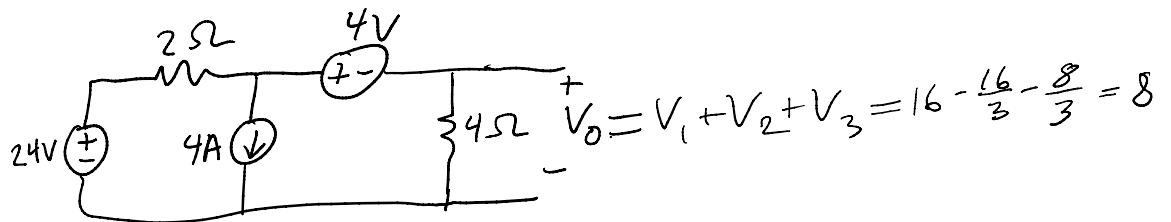

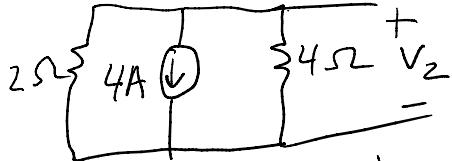
$$V_1 = 24 \left(\frac{4}{6} \right) = 16 \text{ V}$$



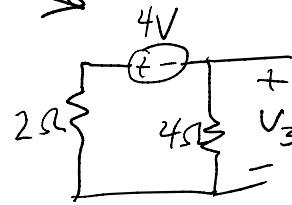
$$V_2 = -4 \left(\frac{2(4)}{2+4} \right) = -\frac{16}{3}$$



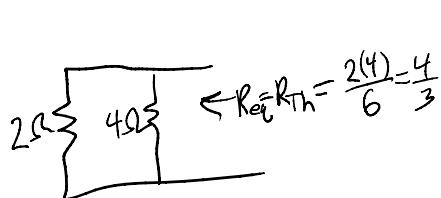
$$V_3 = 4 \left(\frac{4}{6} \right) = \frac{8}{3}$$



$$V_o = V_{Th} = 8$$

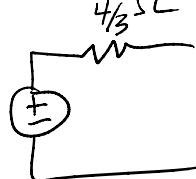

1st and 2nd Order Circuits

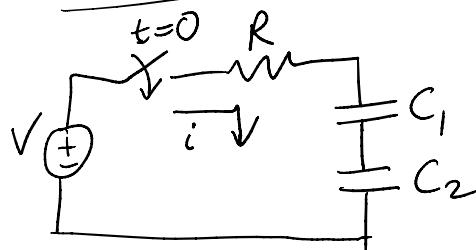

$$V = iR + \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt$$

$$0 = \frac{di}{dt} R + \left(\frac{1}{C_1} + \frac{1}{C_2} \right) i$$

$$i = K e^{st} \quad \frac{di}{dt} = K s e^{st}$$

$$RK s e^{st} + \left(\frac{1}{C_1} + \frac{1}{C_2} \right) K e^{st} = 0$$

$$K e^{st} \left(R_s + \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \right) = 0$$

$$K e^{st} \left(R_s + \left(\frac{C_2 + C_1}{C_1 C_2} \right) \right) = 0$$


$$K e^{st} \left(s + \left(\frac{C_1 + C_2}{R C_1 C_2} \right) \right) = 0$$

$$s = - \left(\frac{C_1 + C_2}{R C_1 C_2} \right) = - \frac{1}{R \left(\frac{C_1 C_2}{C_1 + C_2} \right)}$$

$$\begin{aligned} i &= \frac{V}{R} e^{-R \left(\frac{C_1 C_2}{C_1 + C_2} \right)} \\ i &= \frac{V}{R} \end{aligned}$$

I shared so $Q_1 = Q_2$
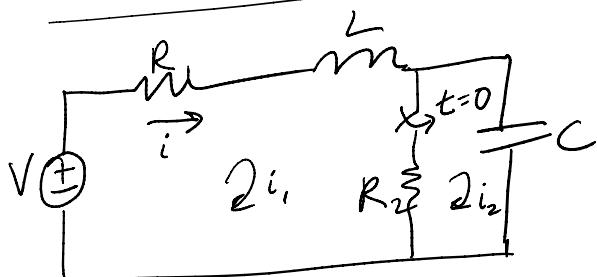
$$\begin{aligned} V_{c_1} &= \frac{1}{C_1} \int i dt \\ V_{c_2} &= \frac{1}{C_2} \int i dt \\ V_{c_1} &= (V - V_{c_2}) \frac{C_2}{C_1} \\ V_c &= V_{c_1} + V_{c_2} \\ V_{c_1} \left(1 + \frac{C_2}{C_1} \right) &= V \frac{C_2}{C_1} \\ V_{c_1} &= V \frac{C_2}{C_1} \cdot \frac{C_1}{C_1 + C_2} = V \frac{C_2}{C_1 + C_2} \end{aligned}$$



$$i_1 = i$$

$$\begin{aligned} i &\stackrel{?}{=} K e^{st} \\ \frac{di}{dt} &= K s e^{st} \\ \frac{d^2i}{dt^2} &= K s^2 e^{st} \end{aligned}$$

$$D > 0$$

2 real values for s

$$s_1, s_2$$

$$i = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

$$\begin{aligned} D &= 0 \\ 1 \text{ real } s \\ s \end{aligned}$$

$$i = K_1 e^{st} + K_2 t e^{st}$$

$$D < 0$$

2 complex values for s

$$s_1 = s_2^*$$

$$j = \sqrt{-1}$$

$$s_1 = r + \omega j$$

$$e^{jx} = \cos(x) + j \sin(x)$$

$$i = e^{rt} (K_1 \cos(\omega t) + j K_2 \sin(\omega t))$$

$$i_{0-} = 0 \quad i_{\infty} = \frac{V}{R_1 + R_2}$$

$$i_{0+} = 0 \quad i_{R2,0+} = \frac{V}{R_2}$$

$$\left(V = i_1 R_1 + L \frac{di_1}{dt} + R_2 (i_1 - i_2) \right) \rightarrow i_2 = \frac{i_1 R_1 + L \frac{di_1}{dt} + R_2 i_1 - V}{R_2}$$

$$R_2 \frac{di_1}{dt} - R_2 \frac{di_2}{dt} = \frac{1}{C} i_2$$

$$R_2 \frac{di_1}{dt} - R_2 \left(\frac{di_1(R_1)}{dt(R_2)} + \frac{L}{R_2} \frac{di_1^2}{dt^2} + \frac{di_1}{dt} \right) = i_1 \frac{R_1}{CR_2} + \frac{L}{CR_2} \frac{di_1}{dt} + \frac{i_1}{C} - \frac{V}{CR_2}$$

$$\underbrace{\frac{L}{R_2} \frac{d^2i}{dt^2}}_{a_1} - \underbrace{\left(\frac{R_2^2 V - R_1 R_2 - L}{R_2} \right) \frac{di}{dt}}_{a_2} + \underbrace{\frac{R_1 + R_2}{R_2 C} i}_{a_3} = 0$$

$$a_1 s^2 + a_2 s + a_3 = 0$$

$$s = \frac{-a_2 \pm \sqrt{a_2^2 - 4a_1 a_3}}{2a_1}$$

$$D = a_2^2 - 4a_1 a_3$$