


## Part 2 (Graded)

### Q1. Textbook Problem 9.40


The circuit shown in Figure P9.40(a) is a type of logic gate. Assume that the diodes are ideal. The voltages  $V_A$  and  $V_B$  independently have values of either 0V (for logic 0, or low) or 5V (for logic 1, or high). For which of the four combinations of input voltages is the output high (i.e.,  $V_O = 5V$ )? What type of logic gate is this? Repeat for the circuit of Figure P9.40(b).

Forward bias = short circuit

Reverse bias = open circuit

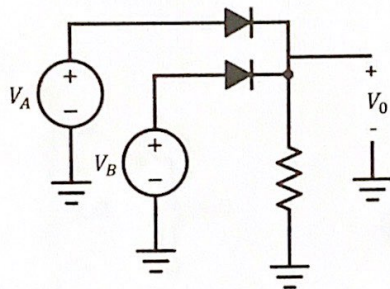

(a)

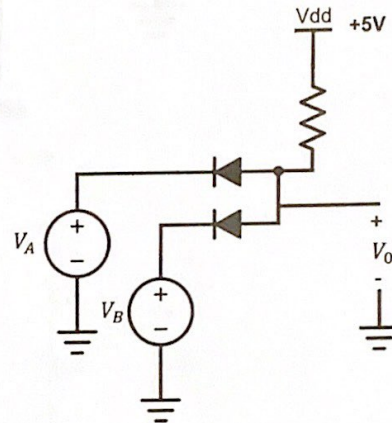

(b)

Figure 9.40

a)

$V_A$	$V_B$	$V_O$
Low open	Low open	0
Low open	High short	1
High short	Low open	1
High short	High short	1

b)

$V_A$	$V_B$	$V_O$
Low short	Low short	0
Low short	High open	0
High open	Low short	0
High open	High open	1

$V_A$	$V_B$	(a) $V_O$	(b) $V_O$
Low	Low	Low (0)	Low
Low	High	High (5)	Low
High	Low	High (5)	Low
High	High	High (5)	High

↓  
OR Gate

↓  
AND Gate

## Q2. Textbook Problem 9.66

Sketch the transfer characteristic ( $v_o$  versus  $v_{in}$ ) to scale for the circuit shown in Figure P9.66. Allow  $v_{in}$  to range from  $-5V$  to  $+5V$  and assume that the diodes are ideal.


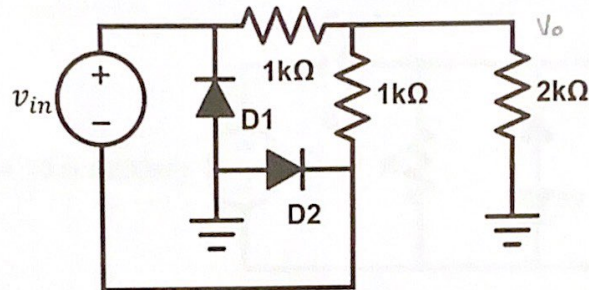


Figure P9.66

$$0 < v_{in} < 5V$$

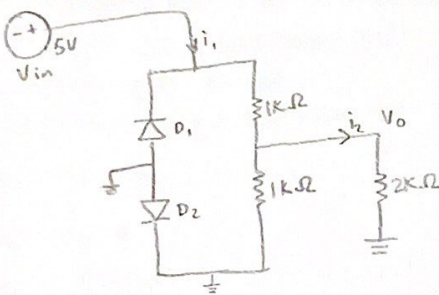

$$V_o = 2000 i_2$$


$$R_{eq} = 1000 + \frac{1000 \times 2000}{1000 + 2000} = 1666.67 = \frac{5}{3} k$$

$$i = \frac{V_{in}}{R_{eq}} = \frac{3}{5} V_{in}$$

$$i_2 = \frac{i}{2+1} \times 1 = \frac{V_{in}}{5k}$$

$$V_o = \frac{2}{5} V_{in} V$$

$$-5V < v_{in} < 0$$

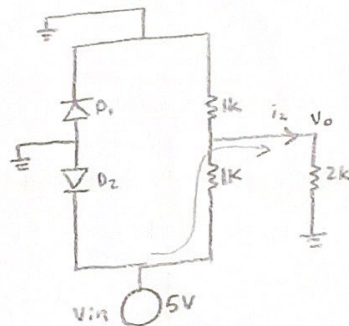

$$V_o = 2000 i_2$$


$$R_{eq} = \frac{5}{3} k$$

$$i_2 = \frac{V_{in}}{\frac{5}{3} k} \times \frac{1}{3} = \frac{V_{in}}{5k}$$

$$V_o = \frac{2}{5} V_{in} V$$

$$V_o = \begin{cases} \frac{2}{5} |V_{in}| & 0 < v_{in} < 5 \\ \frac{2}{5} |V_{in}| & -5 < v_{in} < 0 \end{cases}$$

Add your sketch here:

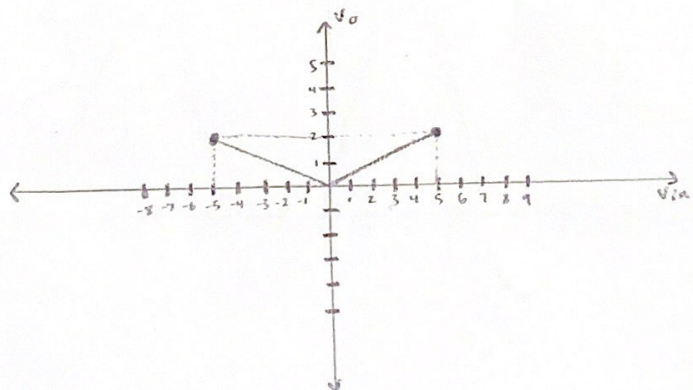



## Q3. Textbook Problem 9.70

Sketch to scale the steady-state output waveform for the circuit shown in Figure P9.70. Assume that  $RC$  is much larger than the period of the input voltage and that the diodes are ideal.


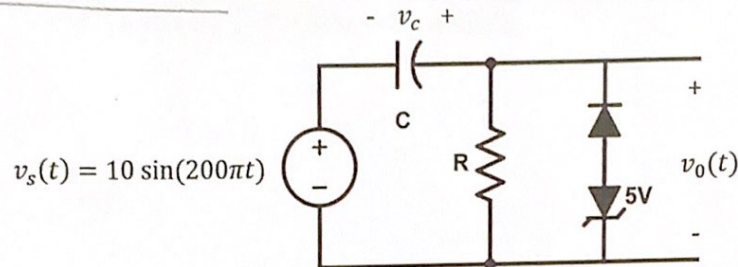


Figure P9.70

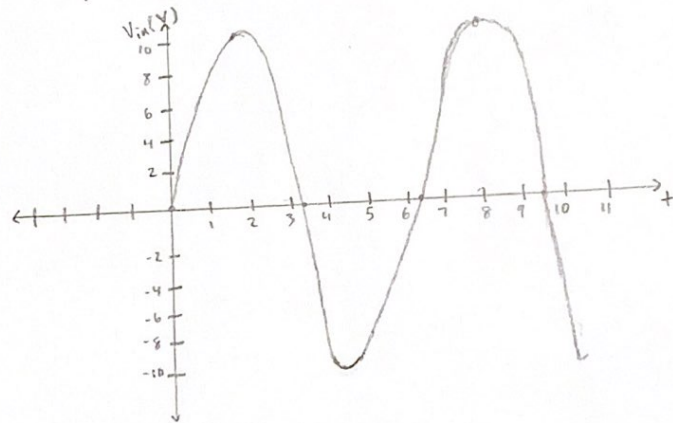Input Waveform (tried my best to sketch it nicely)



For the negative peak of the sinusoidal input:

- If output voltage falls below  $-5V$ , capacitor gets charged
- capacitor can not drop below  $-5V$

$$V_o = V_s + V_c$$

$$V_c = V_o - V_s$$

$$V_c = -5 - (-10)$$

$$V_c = 5V \text{ [capacitor voltage]}$$

$$V_o = V_s(t) + V_c$$

$$V_o = 10 \sin(200\pi t) + 5 \text{ [output voltage]}$$

Negative peak of output voltage

$$V_o = 10 \sin(200\pi t) + 5$$

(negative peak occurs at  $-10V$ )

$$V_o = -10 + 5$$


$$V_o = -5V$$

Positive peak of output voltage  
(positive peak occurs at  $10V$ )

$$V_o = 10 + 5$$

$$V_o = 15V$$

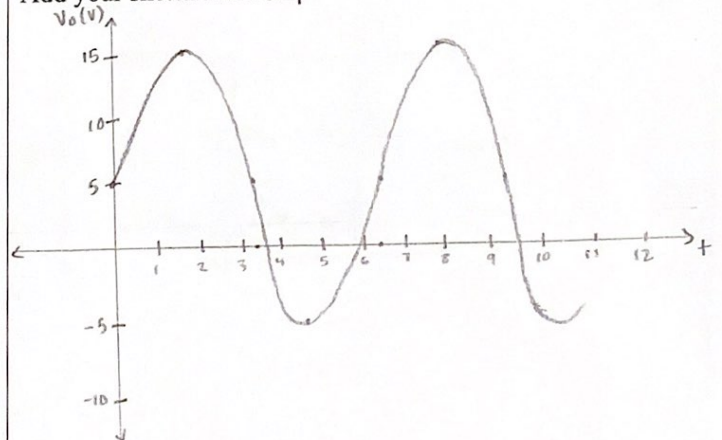
Add your sketch here: Output Waveform (I tried to draw it like)




## Q4. Textbook Problem 9.72

Design a clipper circuit to clip off the portions of an input voltage that fall above 3V or below -5V. Assume that diodes having a constant forward drop of 0.7V are available. Ideal Zener diodes of any breakdown voltage required are available. DC voltage sources of any value are available.

## Basic Clipper Circuit Design

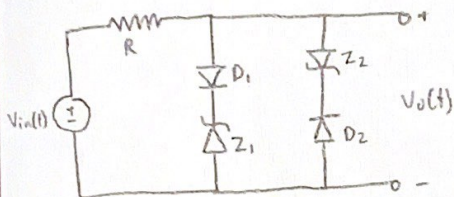

## Positive Cycle

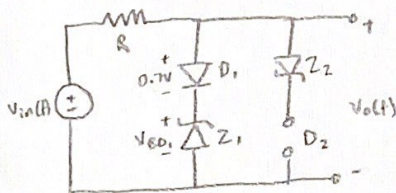

$$V_o(t) = V_{D1} + V_{BD1}$$


$$V_o = 3V$$

$$V_{D1} = 0.7V$$

$$3 = 0.7 + V_{BD1}$$

$$V_{BD1} = 2.3V \Rightarrow 3V \text{ output}$$

## Negative Cycle

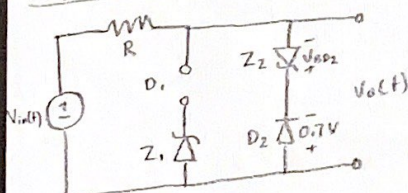

$$V_o(t) = -V_{BD2} - V_{D2}$$

$$V_o = -5V$$

$$V_{D2} = 0.7V$$

$$-5 = -0.7 - V_{BD2}$$

$$V_{BD2} = 4.3V \Rightarrow -5V \text{ output}$$

Combine positive and negative  $\Rightarrow$

Answer:

