

Q1. Fig 1 below shows 2 equivalent circuits (a) and (b). In circuit (a) the 2 coupled inductors have self- inductances L_1 and L_2 as shown and a mutual inductance M . Find L_A , L_B and L_C in terms of L_1 , L_2 and M


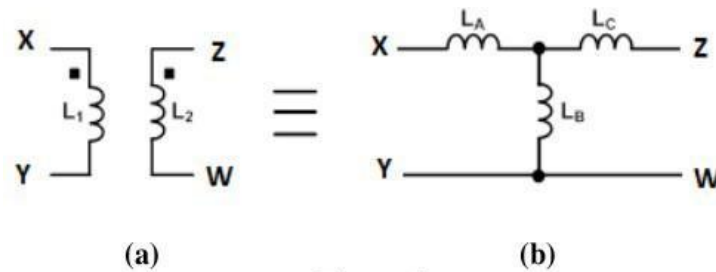


Figure 1

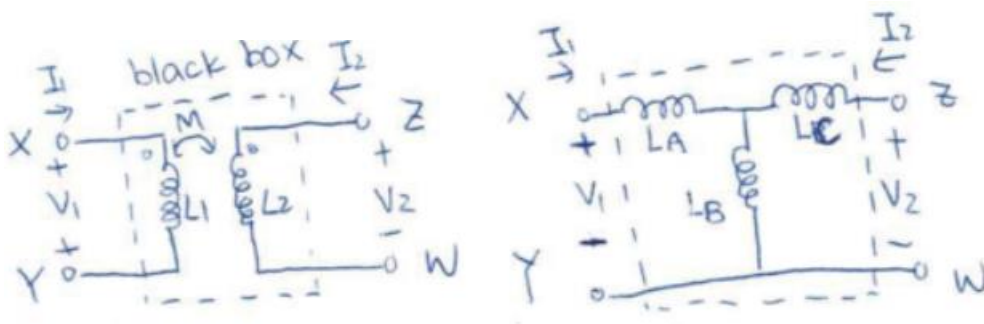

In (a), $V_1 = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$ and $V_2 = L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt}$

In (b), the current through L_B is $I_1 + I_2$, hence

$$V_1 = L_A \frac{dI_1}{dt} + L_B \frac{d}{dt}(I_1 + I_2) \text{ and } V_2 = L_C \frac{dI_2}{dt} + L_B \frac{d}{dt}(I_1 + I_2)$$

To make (a) and (b) equivalent, we will have

$$L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt} = L_A \frac{dI_1}{dt} + L_B \frac{d}{dt}(I_1 + I_2) \text{ and } L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} = L_C \frac{dI_2}{dt} + L_B \frac{d}{dt}(I_1 + I_2)$$

$$\text{So } L_1 = L_A + L_B, M = L_B, L_2 = L_C + L_B$$

$$L_A = L_1 - M$$

$$L_B = M$$

$$L_C = L_2 - M$$

Q2. Use a series of source transformations to find the current i_o in the circuit given in the Fig 2 below.



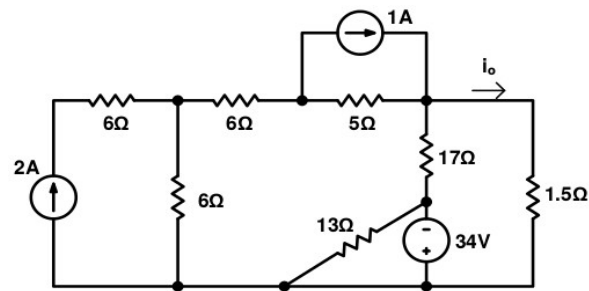


Figure 2

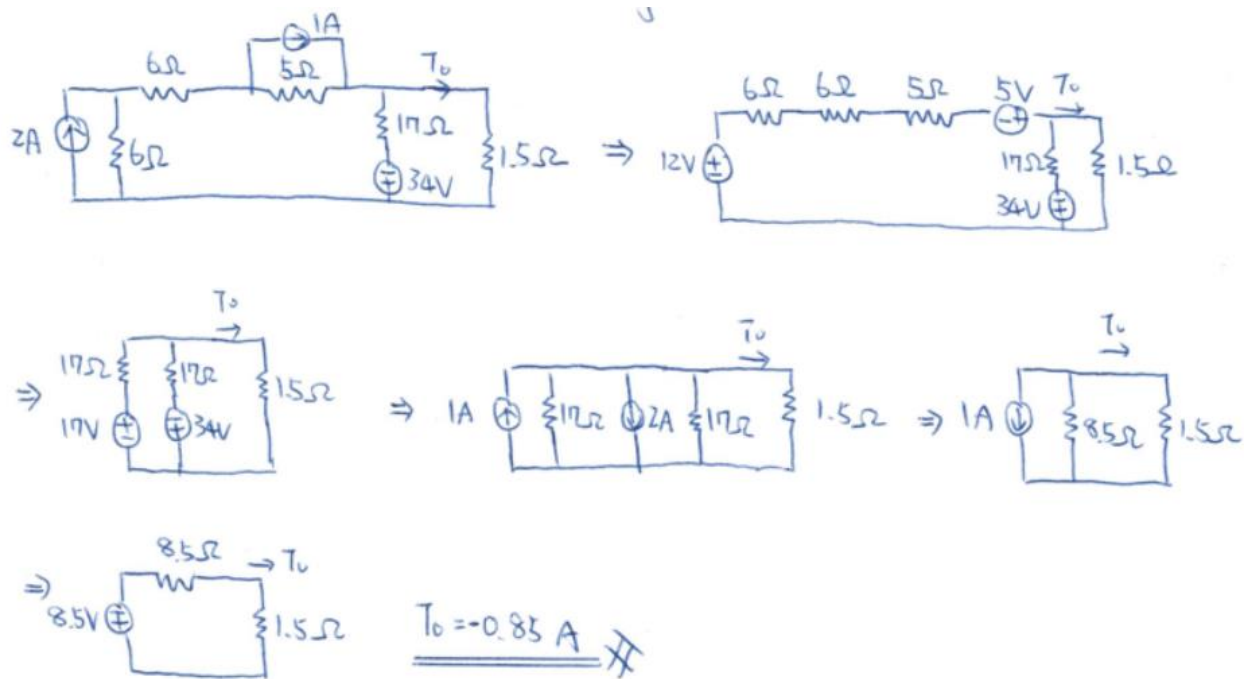We can eliminate the resistor in series with 2A current source and the resistor in parallel with the 34V voltage source. After three times of voltage/current conversion, we have $I_o = -0.85A$




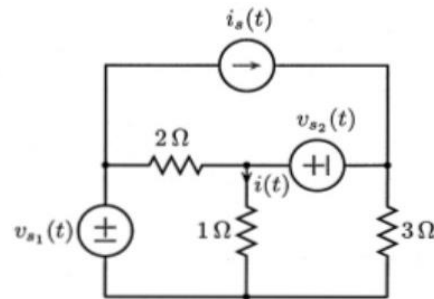Q3. Refer circuit below. Find $i(t)$ (current flowing through the 1 ohm resistor) in terms of $i_s(t)$, $v_{s1}(t)$, $v_{s2}(t)$.



Use mesh current analysis, we have three loops of current I_1, I_2, I_3

3)

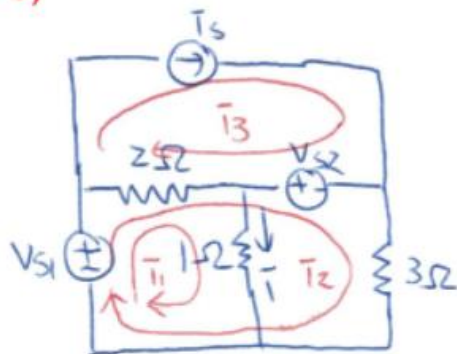

Apply KVL to \bar{I}_1 and \bar{I}_2 loop.

$$\bar{I}_3 = \bar{I}_s$$

$$-V_{s1} + (\bar{I}_1 + \bar{I}_2 - \bar{I}_3) \cdot 2 + \bar{I}_1 = 0$$

$$-V_{s1} + (\bar{I}_1 + \bar{I}_2 - \bar{I}_3) \cdot 2 + V_{s2} + \bar{I}_2 \cdot 3 = 0$$


$$\Rightarrow \begin{cases} 3\bar{I}_1 + 2\bar{I}_2 - 2\bar{I}_3 = V_{s1} & \text{--- (1)} \\ 2\bar{I}_1 + 5\bar{I}_2 - 2\bar{I}_3 = V_{s1} - V_{s2} & \text{--- (2)} \end{cases}$$

$$\textcircled{1} \times 5 - \textcircled{2} \times 2$$

$$\Rightarrow 11\bar{I}_1 - 6\bar{I}_3 = 3V_{s1} + 2V_{s2}$$

$$\bar{I}_1 = \frac{3V_{s1} + 2V_{s2} + 6\bar{I}_s}{11} \quad \text{XX}$$

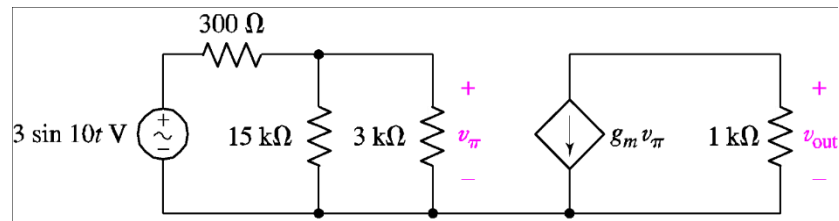Q4. The circuit below is a commonly used equivalent circuit used to model the ac behavior of a bipolar junction transistor amplifier circuit. If $g_m = 38 \text{ m}$, compute v_{out} .



First, we consider the left circuit.

The equivalent parallel resistance is $3 \text{ k}\Omega \parallel 15 \text{ k}\Omega = 2.5 \text{ k}\Omega$

Use voltage divider, we got $V_\pi = 3 \sin 10t * \frac{2.5 \text{ k}\Omega}{2.5 \text{ k}\Omega + 300 \Omega} = 2.68 \sin 10t$

Hence, the dependent source $g_m V_\pi = 0.038 * 2.68 \sin 10t = 0.1018 \sin 10t \text{ A}$

$V_{\text{out}} = -(g_m V_\pi * 1 \text{ k}\Omega) = -101.8 \sin 10t \text{ V}$