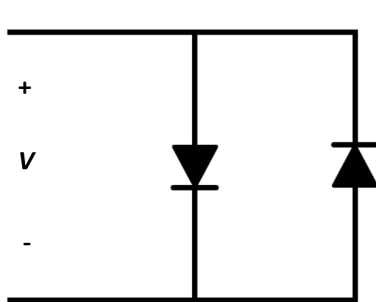


HW5 Solutions


Part 1 (Practice Problems):

Q1. Textbook Problem 9.6


Sketch i versus v to scale for the circuits shown in Figure P9.6. The reverse-breakdown voltages of the Zener diodes are shown. Assume voltages of 0.6V for all diodes including the Zener diodes when current flows in the forward direction.



(a)

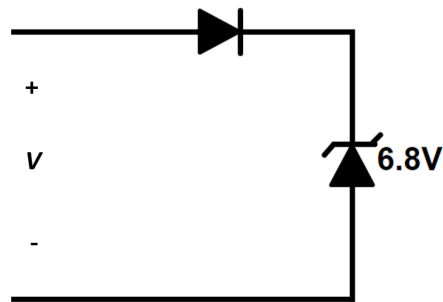




(b)

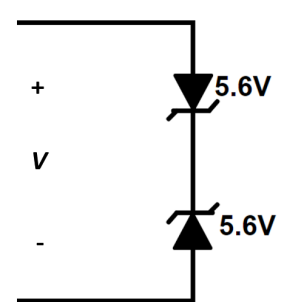

(c)

Figure P9.6

Solution:

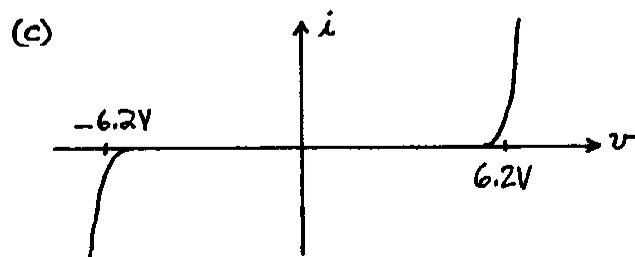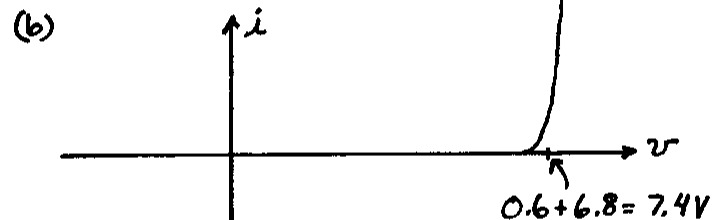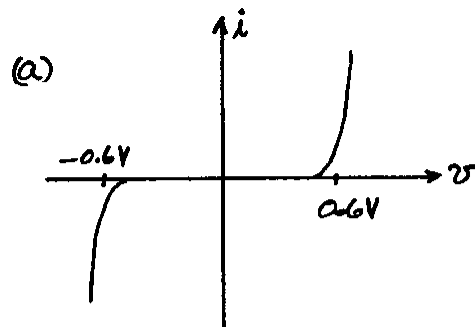

Q2. Textbook Problem 9.37

Find the values of I and V for the circuits of Figure P9.37, assuming that the diodes are ideal.

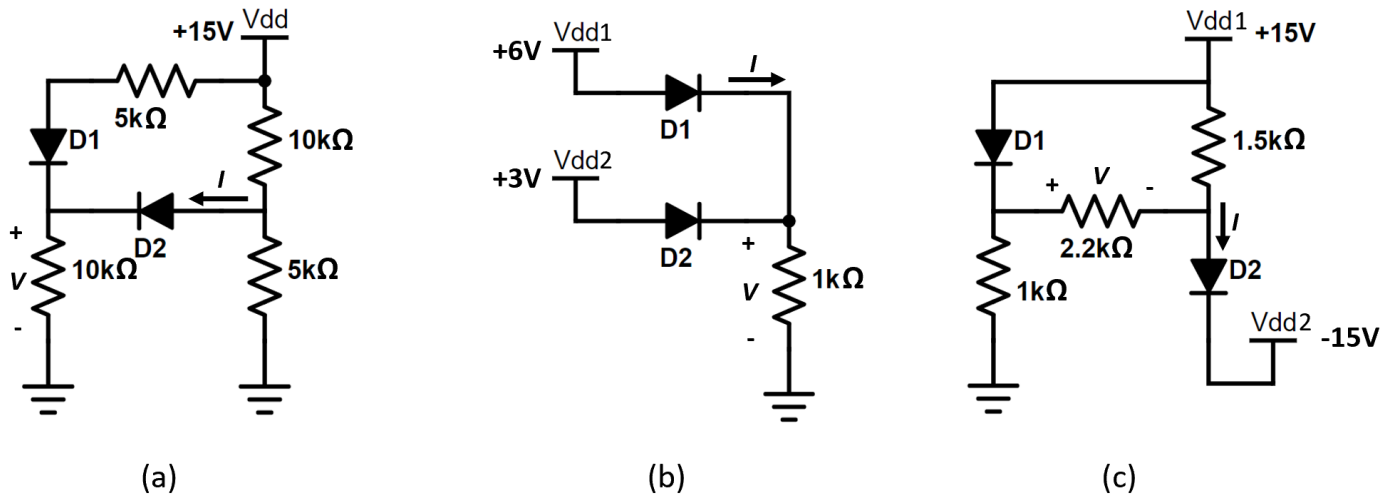


Figure P9.37

Solution:

- (a) D_1 is on and D_2 is off. $V = 10\text{V}$ and $I = 0\text{A}$.
- (b) D_1 is on and D_2 is off. $V = 6\text{V}$ and $I = 6\text{mA}$.
- (c) Both D_1 and D_2 are on. $V = 30\text{V}$ and $I = 33.6\text{mA}$.

Q3. Textbook Problem 9.59

Consider the battery-charging circuit shown in Figure 9.25 on page 476, in which $v_s(t) = 20\sin(200\pi t)$, $R = 80\Omega$, $V_B = 12V$, and the diode is ideal.

- Sketch the current $i(t)$ to scale versus time.
- Determine the average charging current for the battery.

[Hint: The average current is the charge that flows through the battery in one cycle divided by the period.]

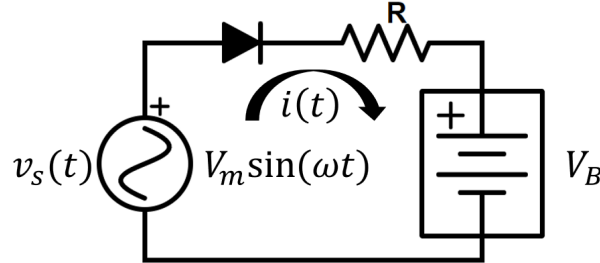


Figure 9.25

Solution:

- (a) The current pulse starts and ends at the times for which

$$\begin{aligned} v_s(t) &= V_B \\ 20 \sin(200\pi t) &= 12 \end{aligned}$$


Solving, we find that

$$\begin{aligned} t_{start} &= \frac{\sin^{-1}(0.6)}{200\pi} = 1.024 \text{ ms} \\ t_{end} &= \frac{T}{2} - t_{start} = 3.976 \text{ ms} \end{aligned}$$

Between these two times, the current is

$$i(t) = \frac{20 \sin(200\pi t) - 12}{80}$$

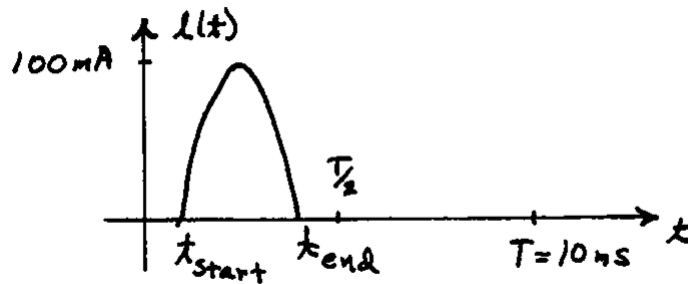A sketch of the current to scale versus time is



- (b) The charge flowing through the battery in one period is

$$\begin{aligned} Q &= \int_{t_{start}}^{t_{end}} i(t) dt = \int_{t_{start}}^{t_{end}} \frac{20 \sin(200\pi t) - 12}{80} dt = \left[-\frac{1}{800\pi} \cos(200\pi t) - \frac{12t}{80} \right]_{t_{start}}^{t_{end}} \\ Q &= 194 \mu\text{C} \end{aligned}$$

Finally, the average current is the charge divided by the period.

$$I_{avg} = \frac{Q}{T} = \frac{194 \times 10^{-6}}{10 \times 10^{-3}} = 19.4 \text{ mA}$$

Q4. Textbook Problem 9.63

Sketch to scale the output waveform for the circuit shown in Figure P9.63. Assume that the diodes are ideal.


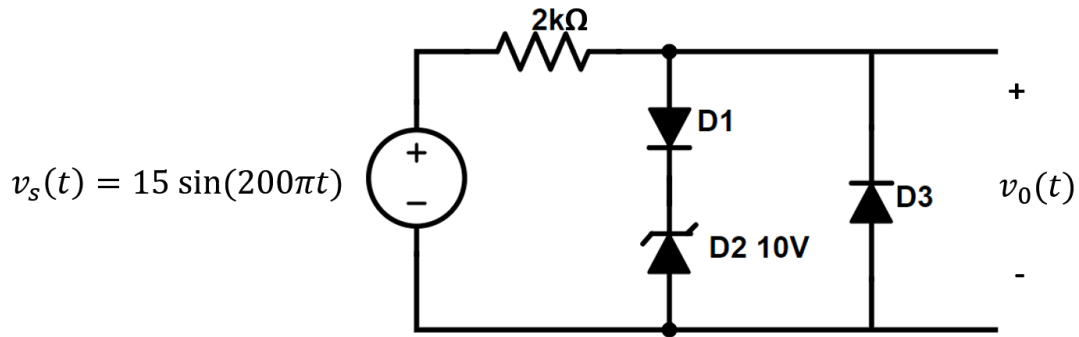


Figure P9.63


Solution:

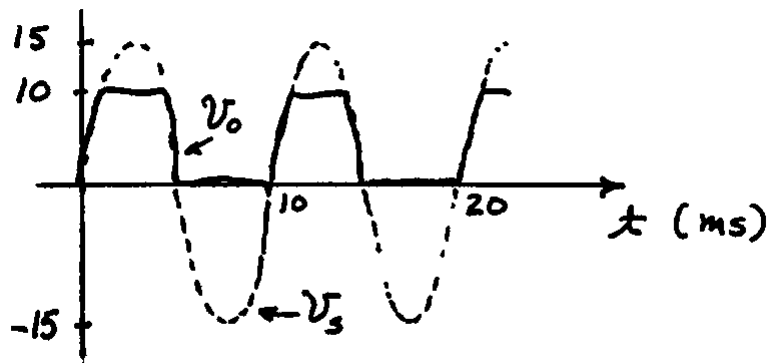When the source voltage is negative, diode D_3 is on and the output $v_o(t)$ is zero. For source voltages between 0 and 10V, none of the diodes conducts and $v_o(t) = v_s(t)$. Finally, when the source voltage exceeds 10V, D_1 is on and D_2 is in the breakdown region so the output voltage is 10V. The waveform is:



Q5. Textbook Problem 9.28

Consider the voltage regulator shown in Figure P9.28. The source voltage V_s varies from 10 to 14V, and the load current i_L varies from 50 to 100mA. Assume that the Zener diode is ideal. Determine the largest value allowed for the resistance R_s so that the load voltage v_L remains constant with variations in load current and source voltage. Determine the maximum power dissipation in R_s .

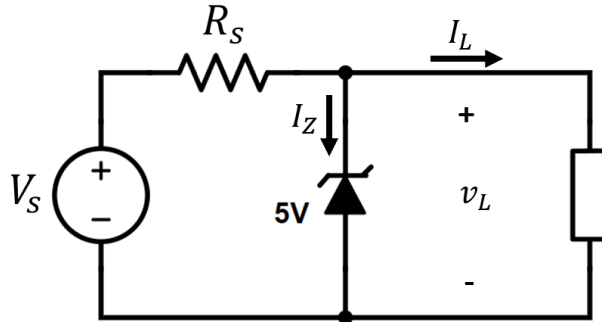**Figure 9.28****Solution:**

We need to choose R_s so the minimum reverse current through the Zener diode is zero. Minimum current through the Zener occurs with minimum V_s and maximum i_L . Also, we can write:

$$i_Z = \frac{V_s - v_L}{R_s} - i_L$$

Substituting values, we have

$$i_Z = 0 = \frac{10 - 5}{R_s} - 0.1$$

Solving for the resistance, we find $R_s = 50\Omega$.

Maximum power dissipation in the resistance occurs for maximum V_s .

$$P_{max} = \frac{(V_{s,max} - v_L)^2}{R_s} = \frac{(14 - 5)^2}{R_s} = 1.62W$$