

## Discussion 2 Notes

Sunday, April 10, 2022 10:33 PM







$$V = IR \quad = \quad I \cdot \frac{V}{R}$$



$$= R_1 \parallel R_2 \quad = \quad R_1 + R_2$$

$$V_1 + V_2 = V_1 + V_2$$


$$I_1 + I_2 = I_1 + I_2$$

### Example

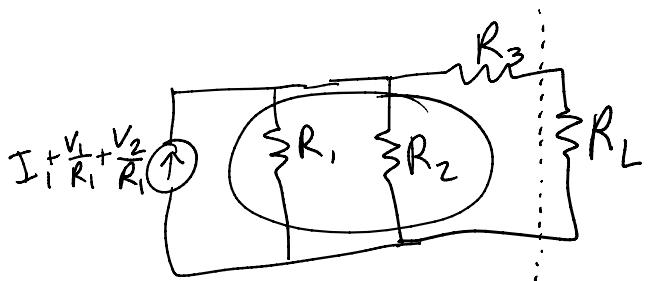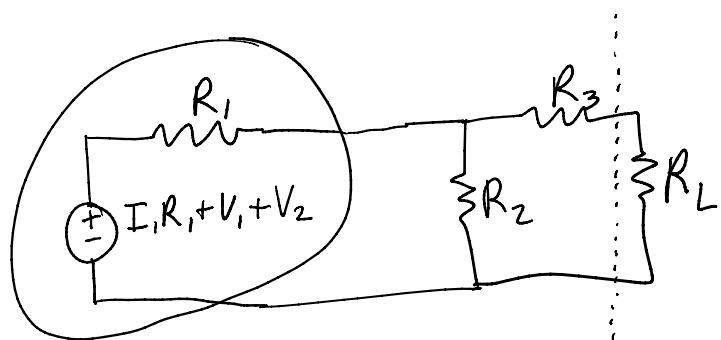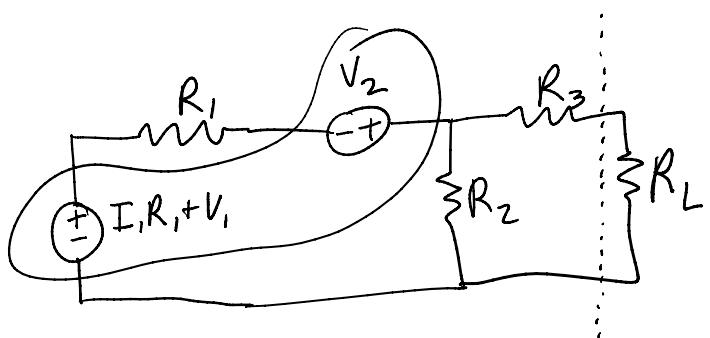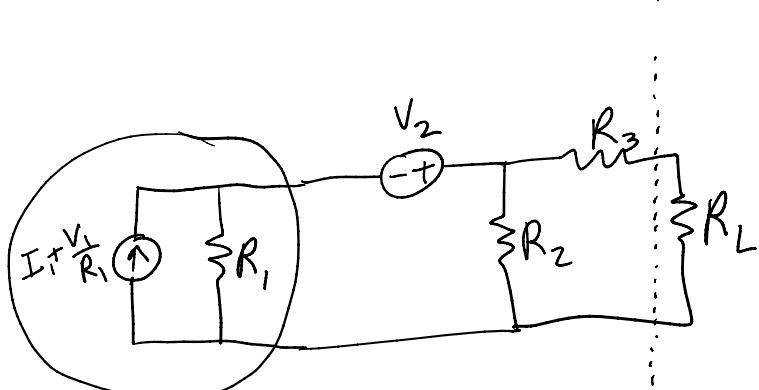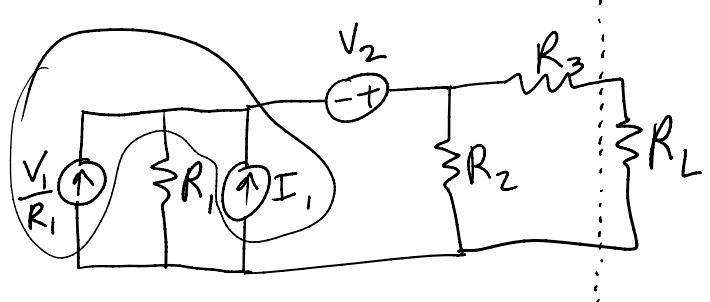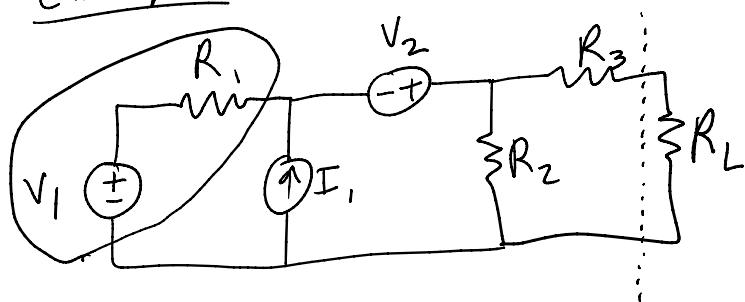

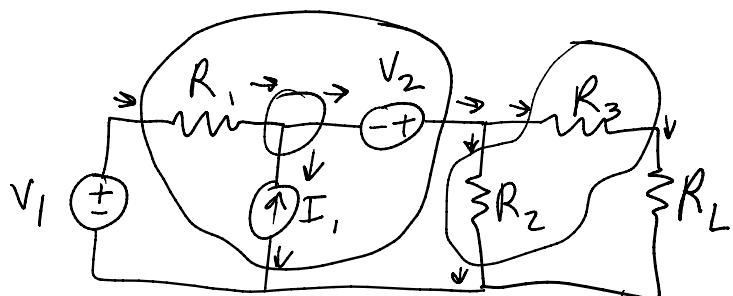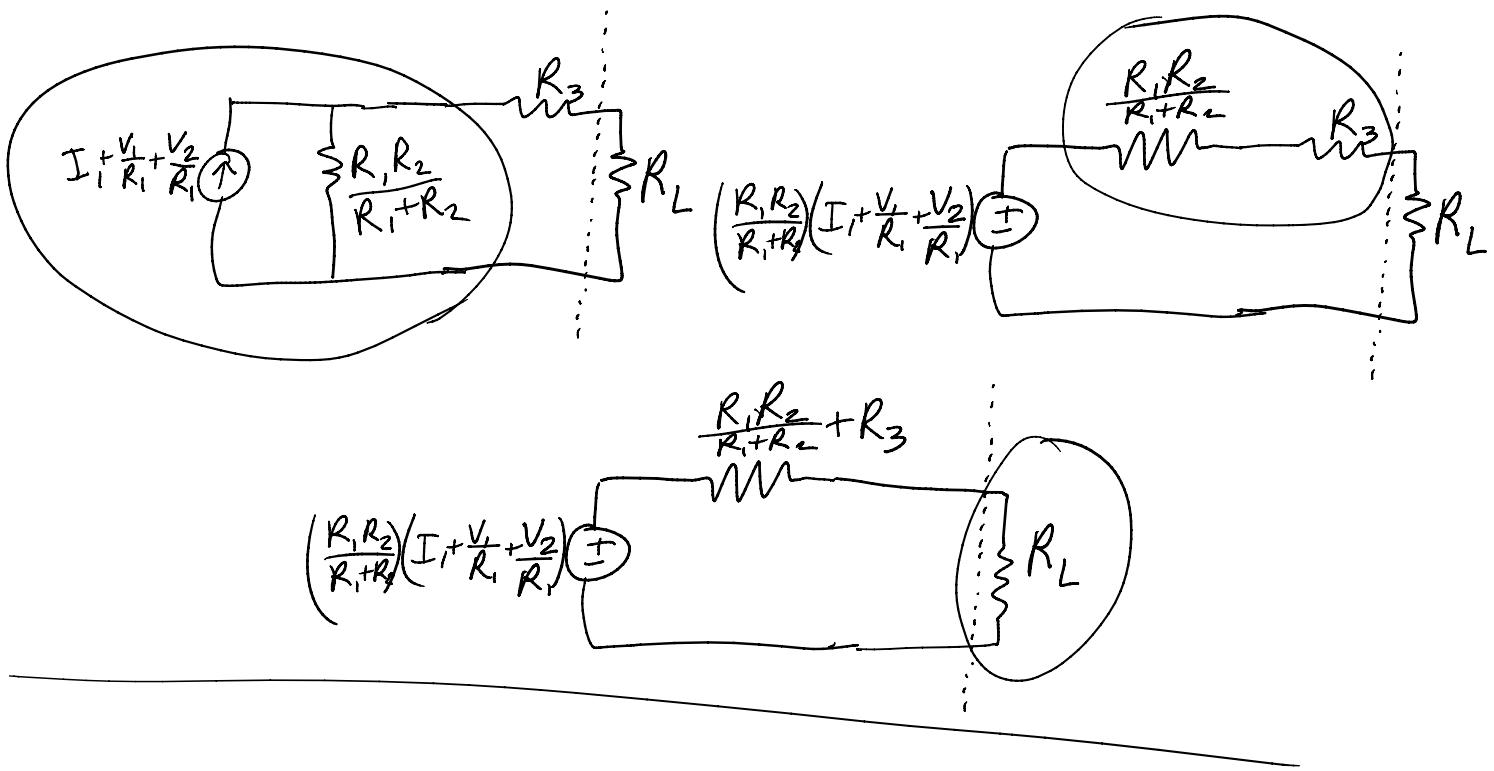

Example:

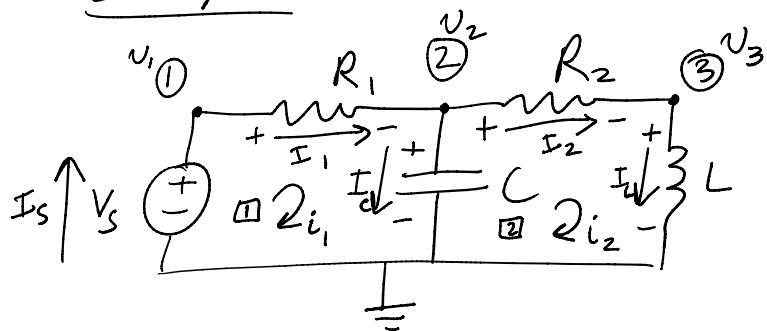

KVL:

$$\boxed{1} \quad V_s = I_1 R_1 + \frac{1}{C} \int I_c dt$$

$$\boxed{2} \quad \frac{1}{C} \int I_c dt = I_2 R_2 + L \frac{dI_L}{dt}$$

KCL:

$$\textcircled{1} \quad I_S = \frac{V_1}{R_1}$$

$$\textcircled{2} \quad \frac{V_1}{R_1} = \frac{V_2}{R_2} + C \frac{dV_C}{dt}$$

$$\textcircled{3} \quad \frac{V_2}{R_2} = \frac{1}{L} \int V_L dt$$

$$\begin{aligned} I_c &= C \frac{dV_C}{dt} & V_L &= L \frac{dI_L}{dt} \\ \frac{1}{C} \int I_c dt &= V_C & \frac{1}{L} \int V_L dt &= I_L \end{aligned}$$

$$I_C = i_1 - i_2$$

KVL:

$$\boxed{1} \quad V_S = I_1 R_1 + \frac{1}{C} \int I_C dt \rightarrow V_S = i_1 R_1 + \frac{1}{C} \int i_1 - i_2 dt$$

$$\boxed{2} \quad \frac{1}{C} \int I_C dt = I_2 R_2 + L \frac{d I_L}{dt} \rightarrow 0 = i_2 R_2 + L \frac{d i_2}{dt} - \frac{1}{C} \int i_1 - i_2 dt$$

### Mesh Current Analysis

$$\begin{bmatrix} V_S \\ 0 \end{bmatrix} = \begin{bmatrix} R_1 + \frac{1}{C} \int dt & -\frac{1}{C} \int dt \\ -\frac{1}{C} \int dt & R_2 + L \frac{d}{dt} + \frac{1}{C} \int dt \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

KCL:

$$\textcircled{1} \quad I_S = \frac{V_1}{R_1} \rightarrow I_S = \frac{V_1 - V_2}{R_1}$$


$$\textcircled{2} \quad \frac{V_1}{R_1} = \frac{V_2}{R_2} + C \frac{d V_C}{dt} \rightarrow 0 = -\frac{V_1 - V_2}{R_1} + \frac{V_2 - V_3}{R_2} + C \frac{d V_2}{dt}$$

$$\textcircled{3} \quad \frac{V_2}{R_2} = \frac{1}{L} \int V_L dt \rightarrow 0 = -\frac{V_2 - V_3}{R_2} + \frac{1}{L} \int V_3 dt$$

### Node Voltage Analysis

$$\begin{bmatrix} I_S \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} & -\frac{1}{R_1} & 0 \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + C \frac{d}{dt} & -\frac{1}{R_2} \\ 0 & -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{L} \int dt \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

### Additional Problem

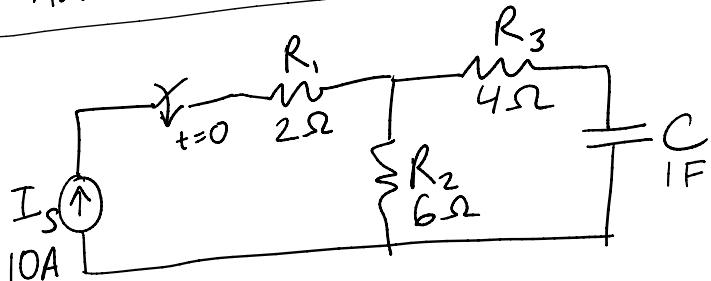

$$t=t_1, I_2 = 5A$$

$$V_{C,t1} = 10V$$

$$V_{R_1,t1} = 20V$$

$$V_{R_2,t1} = 30V$$

$$V_{R_3,t1} = 20V$$

$$V_{R_4,t1} = 20V$$

$$t=t_2, I_3 = 1A$$

$$V_{C,t2} = 50V$$

$$V_{R_1,t2} = 20V$$

$$V_{R_2,t2} = 9 \cdot 6 = 54V$$


$$V_{R_3,t2} = 4V$$

$$V_{C,0+} = 0$$

$$V_{R_1,0+} = 2 \cdot 10 = 20V$$

$$V_{R_2,0+} = 4 \cdot 6 = 24V$$

$$V_{R_3,0+} = 6 \cdot 4 = 24V$$

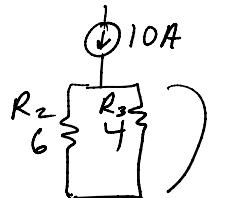

$$I_2 \cdot 6 = I_3 \cdot 4$$

$$\frac{I_2}{I_2 + I_3} = \frac{2}{3}$$

$$\frac{2}{3} I_3 = 10$$

$$I_3 = 6$$

$$I_2 = 4$$