

Direct Current (DC)

$$V = 5V, I = 1A$$



120VAC, 60Hz
(110-120) (50-60)

RMS Voltage



$$P = \frac{V^2}{R}$$

Alternating Current (AC)

$$V = 5\sin(\omega t), I = \cos(\omega t)$$

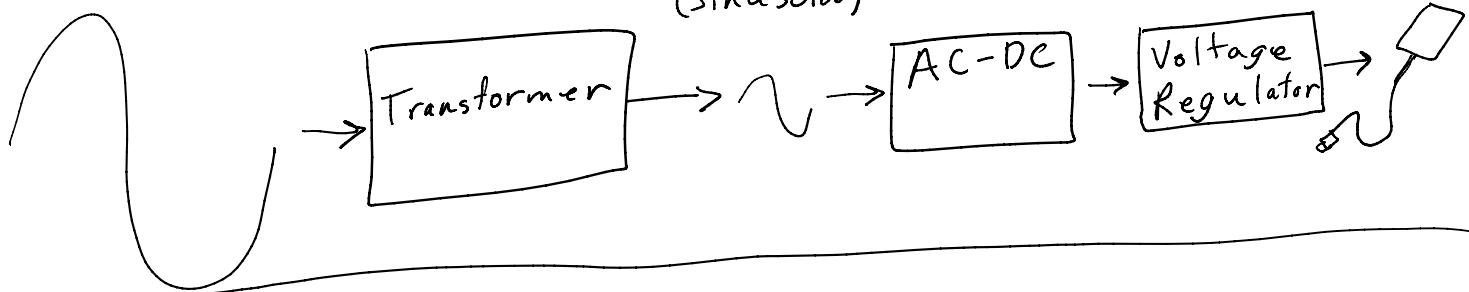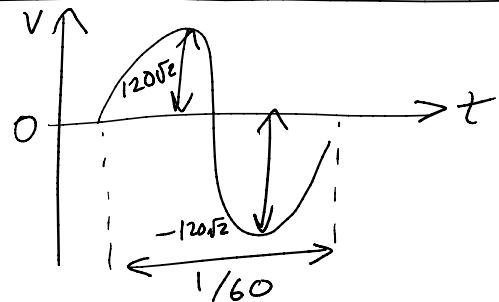
Ideal Transformer

$$V_2 = \frac{N_2}{N_1} V_1, i_2 = -\frac{N_1}{N_2} i_1$$

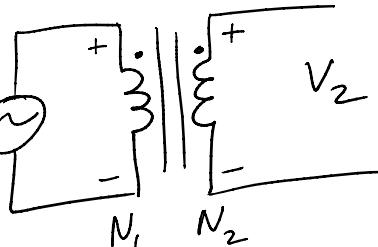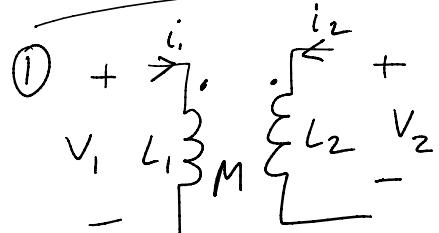Mutual Inductance

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
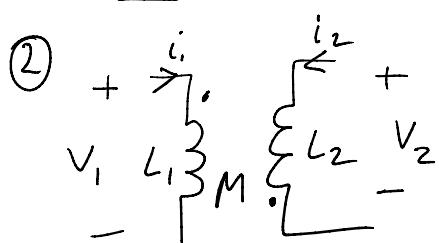
$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$



$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

③


$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

④

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
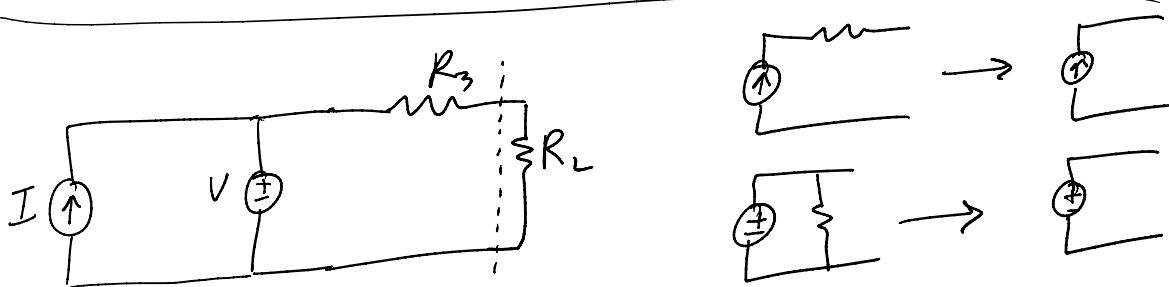
$$V_2 = -L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$



Voltage Divider

$$I = \frac{V_{in}}{R_1 + R_2}$$


$$V_{out} = I R_2 = \frac{V_{in} R_2}{R_1 + R_2}$$

Current Divider


$$V = I \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{V}{R_1} = I \frac{R_2}{R_1 + R_2}$$
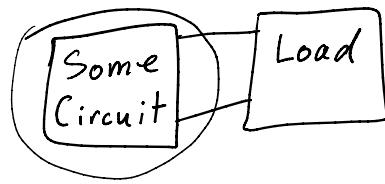
$$I_2 = \frac{V}{R_2} = I \frac{R_1}{R_1 + R_2}$$




Thevenin

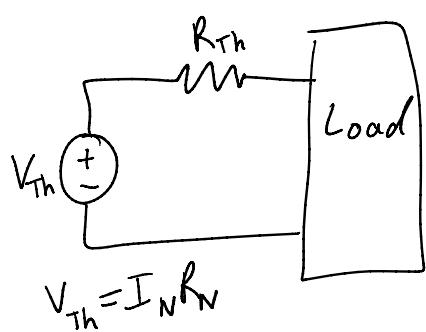


$$R_{Th} = R_N$$


Norton

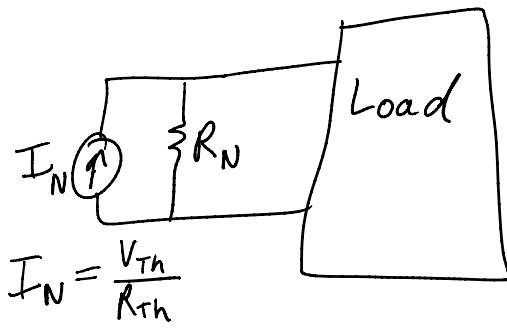

$$I_N = \frac{V_{Th}}{R_{Th}}$$

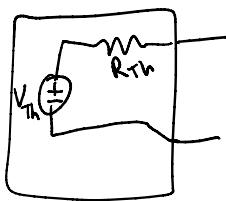


Open Circuit
Voltage
 $V_{oc} = V_{Th}$

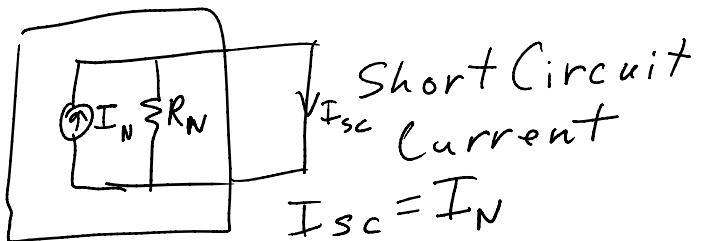

Short Circuit
Current
 $I_{sc} = I_N$

$$\textcircled{+} \textcircled{-} V=0 \rightarrow |$$


$$\textcircled{+} \textcircled{-} I=0 \rightarrow |$$

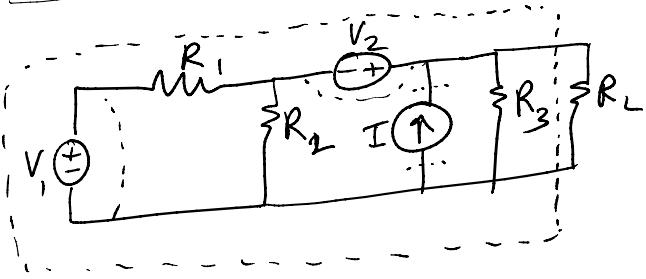

$$\begin{aligned} & \text{Req?} \\ & \text{Req} = R_1 \parallel R_2 \parallel R_3 \\ & R_{Th} = R_N = \text{Req} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \end{aligned}$$

Superposition

V_1 On

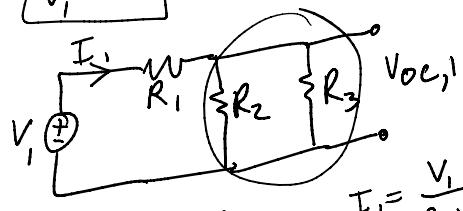

$$V_{oc,1} = V_1 \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}$$

$$I_1 = \frac{V_1}{R_1 + R_2 \parallel R_3}$$

$$V_{oc,1} = V_1 - I_1 R_1$$

$$V_{oc,1} = V_1 - \frac{V_1 R_1}{R_1 + R_2 \parallel R_3}$$

$$V_{oc,1} = V_1 \left(1 - \frac{R_1}{R_1 + R_2 \parallel R_3} \right)$$


$$V_{oc,1} = V_1 \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}$$

$$V_{oc,1} = \frac{V_1 R_2 R_3}{R_1 + R_2 R_3 + R_2 R_3}$$

$$V_{oc,1} = \frac{V_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$V_{oc} = V_{oc,1} + V_{oc,2} + V_{oc,3}$$

V_2 On

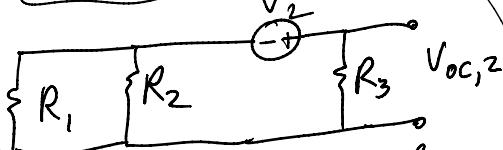

$$V_{oc,2} = V_2 \frac{R_3}{R_3 + R_1 \parallel R_2}$$

$$V_{oc,2} = \frac{V_2 R_3}{R_3 + \frac{R_1 R_2}{R_1 + R_2}}$$

$$V_{oc,2} = \frac{V_2 R_3 (R_1 + R_2)}{R_1 R_3 + R_2 R_3 + R_1 R_2}$$

I On



$$V_{oc,3} = I (R_1 \parallel R_2 \parallel R_3)$$

$$V_{oc,3} = I \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$V_{Th} = V_{oc} = V_{oc,1} + V_{oc,2} + V_{oc,3} = \frac{V_1 R_2 R_3 + V_2 R_3 (R_1 + R_2) + I R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$I_N = \frac{V_{Th}}{R_{Th}}$$