

①

Due Tuesday (4/12) @ 3pm

Ethan Wong

305319001

Dis 1A

ECE 100 HW1

1. i) KCL states that the sum of all currents entering a node

is the same as the sum of all currents leaving a node.

Since $i_1(t)$ is the only current entering N_3 and $i_2(t)$ is the only current leaving N_3 , we know that $i_1(t) = i_2(t)$

$$\text{KCL: } i_1(t) - i_2(t) = 0$$

$$\text{KCL: } \sum i(t) = 0$$

$$i_1(t) = i_2(t) \quad \checkmark$$

ii) KCL can also be applied in this situation.


$$\text{KCL: } \sum i(t) = 0$$

$$i_1(t) - i_2(t) - i_3(t) + i_4(t) = 0$$

$$i_1(t) + i_4(t) = i_2(t) + i_3(t)$$

The result derived from (i) is not necessarily applicable in this situation. The KCL equation now includes $i_3(t)$ and $i_4(t)$ so we can't say for certain that $i_1(t) = i_2(t)$ anymore.

2.

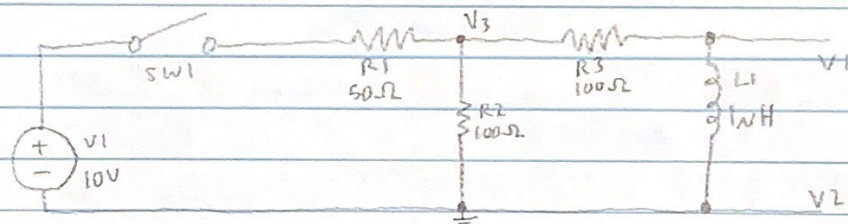

$$V = IR$$

$$10 = I \cdot 50 \quad I = 0.2$$

a) Right when the switch is closed, the inductor ($L1$) still acts as an open circuit because it doesn't change instantly.

Thus $V_3 - V_2$ is essentially the same as the voltage across $R2$.

To find voltage across $R2$, you can kind of ignore right side of the circuit (because it's an open circuit).

$$R1 \text{ is in series with } R2 \rightarrow 50\Omega + 100\Omega = 150\Omega$$

$$V = IR$$

$$10V = I(150\Omega)$$

$$I = 0.0667$$

$$\text{Voltage across } R2: V = IR$$

$$V = 0.0667 \times 100\Omega = 6.67V$$

$$V_3 - V_2 = 6.67V$$

2

b) $t = t_0$ $V_1 - V_2 = 4V$

$V_2 = 0V$, it's connected to ground $V_1 = 4V$

KCL @ V_3

$$\frac{10 - V_3}{50} = \frac{V_3 - 0}{100} + \frac{V_3 - V_1}{100}$$

entering V_3 leaving V_3

$$\frac{10 - V_3}{50} = \frac{V_3}{100} + \frac{V_3 - 4}{100}$$

$$-4V_3 = -24$$

$$V_3 = 6V$$

Next find current through R_3

$$\frac{V_3 - V_1}{100} = \frac{6 - 4}{100} = 0.02A$$

KCL

Current through R_3 flows into L (current entering V_1 = current leaving V_1)

$$i_2(t_0) = 0.02A$$

$$V = L \frac{di_2}{dt}$$

$$4 = 10^{-6} \frac{di_2}{dt} \rightarrow \frac{di_2}{dt} = 4000000 A/s$$


$$i_2(t_0) = 0.02A$$

$$\frac{di_2(t_0)}{dt} = 4000000 A/s$$

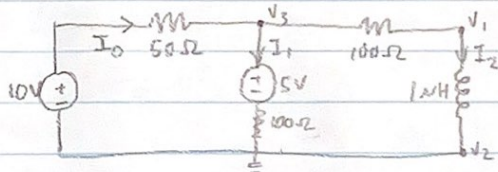c) $t = t_1$ $V_3 - V_2 = 5V$

$V_2 = 0V$, it's connected to ground $V_3 = 5V$ (voltage across R_2 is $5V$)

Think of circuit like this (for visualization purposes):



$$I_0 = \frac{10 - 5}{50} = 0.1A$$

$$I_1 = \frac{5 - 0}{100} = \frac{5}{100} = 0.05A$$

$$I_2 = I_0 - I_1 \rightarrow I_2 = 0.05A$$

$$i_2(t_1) = 0.05A$$

Use KCL at V_3

$$\frac{10 - V_3}{50} = \frac{V_3 - 0}{100} + \frac{V_3 - V_1}{100}$$

$$\frac{10 - 5}{50} = \frac{5}{100} + \frac{5 - V_1}{100}$$

$$V_1 = 0$$

$$V_1 - V_2 = 0$$

$$V = L \frac{di_2}{dt}$$

$$0 = 10^{-6} \frac{di_2}{dt}$$


$$0 = \frac{di_2}{dt}$$

$$0 = \frac{di_2(t_1)}{dt}$$

$$i_2(t_1) = 0.05A$$

$$\frac{di_2(t_1)}{dt} = 0 A/s$$

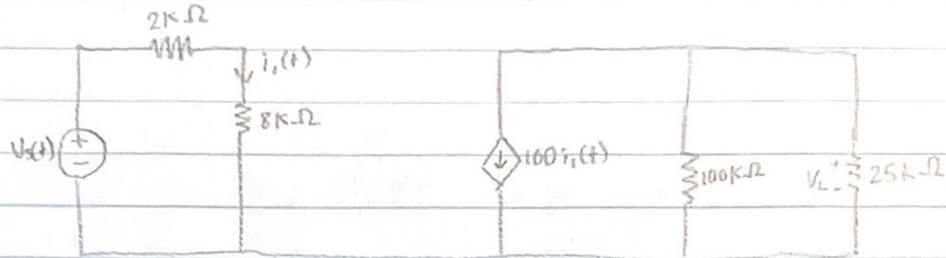3. Express $V_L(t)$ as a function of $V_S(t)$




Ohm's Law: $V = iR$

$$V_S = i_1 (10k\Omega)$$

$$i_1 = \frac{V_S}{10000} \text{ A}$$

Right Side (Equivalent Circuits)

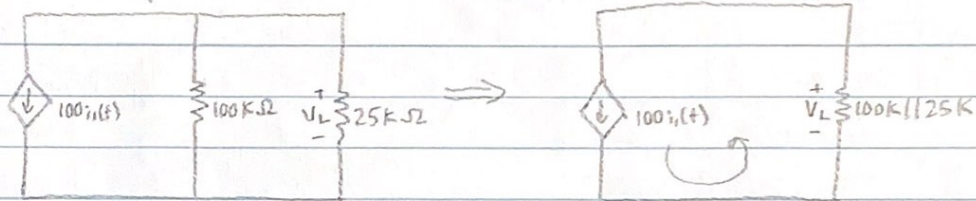

$$100k\Omega || 25k\Omega = \frac{100k\Omega \times 25k\Omega}{100k\Omega + 25k\Omega} = 20k\Omega$$

$$V_L = iR$$

$$V_L = -100i_1(t) \times 20k\Omega$$


$$V_L = -100 \frac{V_S}{10000} \times 20k\Omega$$

$$V_L = \frac{-V_S}{100} \times 20000$$

$$\boxed{V_L = -200V_S}$$

$$V = iR$$

4.

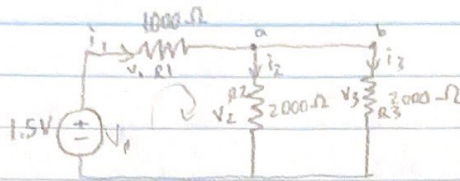

a) Ohm's Law

KVL

$$V_1 = 1000 i_1 \quad 1.5 = 1000 i_1 + 2000 i_2 \quad (1.5 = V_1 + V_2)$$

$$V_2 = 2000 i_2 \quad V_2 = V_3 \quad (i_2 = i_3 \text{ bc node a and node b are same})$$

$$V_3 = 2000 i_3$$

$$\text{KCL: } i_1 = i_2 + i_3$$

entering node a leaving node a (node a and node b are equivalent)

b) $V_2 = V_3$

$$2000 i_2 = 2000 i_3 \rightarrow i_2 = i_3 \quad \checkmark$$

$$i_1 = i_2 + i_3$$

$$i_1 = 2 i_2 \quad \checkmark$$

$$1.5 = 1000 i_1 + 2000 i_2$$

$$1.5 = 2000 i_2 + 2000 i_2$$

$$1.5 = 4000 i_2$$

$$i_2 = 0.000375 \text{ A} = 0.375 \text{ mA}$$

$$i_1 = 0.75 \text{ mA}$$

$$i_2 = 0.375 \text{ mA}$$

$$i_3 = 0.375 \text{ mA}$$

$$V_1 = 0.75 \text{ V}$$

$$V_2 = 0.75 \text{ V}$$

$$V_3 = 0.75 \text{ V}$$

c) Element Power Absorbed

$P = vi$

$$V_1 \quad 1.5 \times (-i_1) = 1.5 \times (-0.75 \text{ mA}) = -1.125 \text{ mW}$$

$$R_1 \quad V_1 \times (i_1) = 0.75 \text{ V} \times 0.75 \text{ mA} = 0.5625 \text{ mW}$$

$$R_2 \quad V_2 \times (i_2) = 0.75 \text{ V} \times 0.375 \text{ mA} = 0.28125 \text{ mW}$$

$$R_3 \quad V_3 \times (i_3) = 0.75 \text{ V} \times 0.375 \text{ mA} = 0.28125 \text{ mW}$$

$$\text{Total Power Absorbed by Source} = -(\text{Power absorbed from } V_1)$$

$$= 1.125 \text{ mW}$$

$$\text{Total Power Absorbed by Resistors} = 0.5625 \text{ mW} + 0.28125 \text{ mW} + 0.28125 \text{ mW}$$


$$= 1.125 \text{ mW}$$

This shows us that the total power absorbed in the resistors


is equal to the total power supplied by the source. This

means that overall, the circuit absorbed 0 power. (0W)

5.

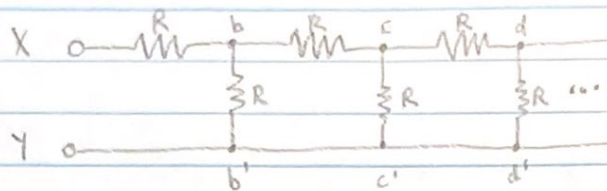

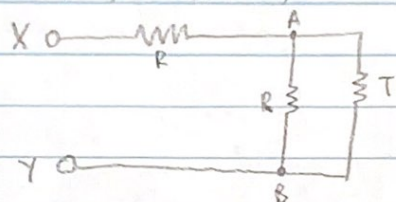
To simplify the circuit, think of it like this:



(T represents equivalent resistance between nodes X and Y)

Now observe that $R \parallel T$

$$R \parallel T = \frac{RT}{R+T}$$

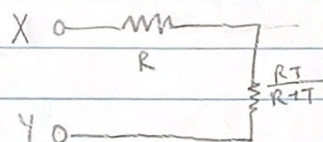

Now the resistors are in series

$$T(R+T)$$

$$T = R + \frac{RT}{R+T}$$

$$TR + T^2$$

$$RT + T^2 = R^2 + 2RT$$

$$T^2 = R^2 + RT$$

$$0 = R^2 - T^2 + RT$$

Solve for T

$$T = \frac{-R \pm \sqrt{5}R}{2} \Rightarrow T = \frac{R + \sqrt{5}R}{2} \Rightarrow T = \left(\frac{1 + \sqrt{5}}{2}\right)R$$

$$T = 1.618R$$

$$R_{eq} = 1.618R$$

The equivalent resistance between X and Y is $1.618R$.