

## HW6

**Due Thursday 6/2 at 3:00PM on Gradescope**

*You are not required to submit the solutions to Part 1, but you still should solve these questions since op amps will be on the final.*

### Part 1 (Practice Problems):

#### Q1. Problem 11.3

A certain NMOS transistor has  $V_{t0} = 1V$ ,  $KP = 50\mu A/V^2$ ,  $L = 5\mu m$ , and  $W = 50\mu m$ . For each set of voltages, state the region of operation and compute the drain current.

- $v_{GS} = 4V$  and  $v_{DS} = 10V$
- $v_{GS} = 4V$  and  $v_{DS} = 2V$
- $v_{GS} = 0V$  and  $v_{DS} = 10V$



**Solution:**

$$KP = \frac{1}{2} KP \left( \frac{W}{L} \right) = 0.25mA/V^2$$

- Saturation because we have  $v_{GS} \geq V_{t0}$  and  $v_{DS} \geq v_{GS} - V_{t0}$ .  
 $i_D = K(v_{GS} - V_{t0})^2 = 2.25mA$
- Triode because we have  $v_{DS} < v_{GS} - V_{t0}$  and  $v_{GS} \geq V_{t0}$ .  
 $i_D = K[2(v_{GS} - V_{t0})v_{DS} - v_{DS}^2] = 2mA$
- Cutoff because we have  $v_{GS} \leq V_{t0}$ .  
 $i_D = 0$

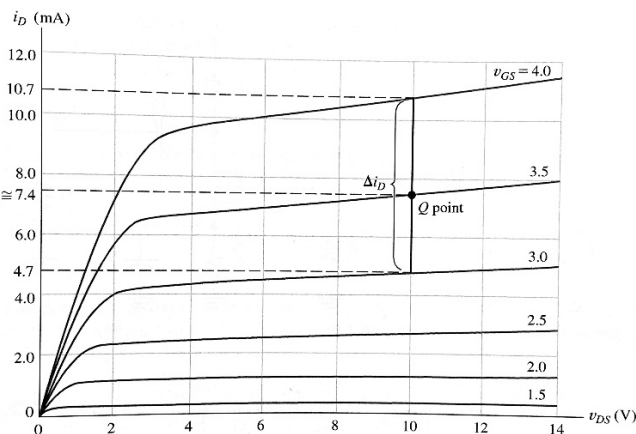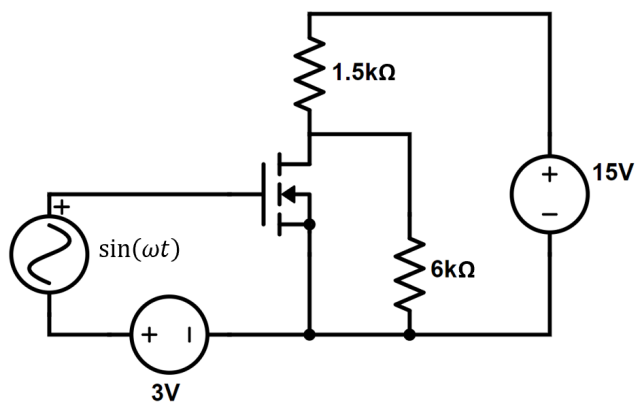
#### Q2. Problem 11.22

Use a load-line analysis of the circuit shown in the figure below to determine the values of  $V_{DSQ}$ ,  $V_{DSmin}$ , and  $V_{DSmax}$ . The characteristics of the FET are shown in the plot on the right. Note that the labelled  $I_{DQ}$  is for a different textbook example, not for this problem. [Hint: First, replace the 15V source and the resistances by their Thevenin equivalent circuit.]



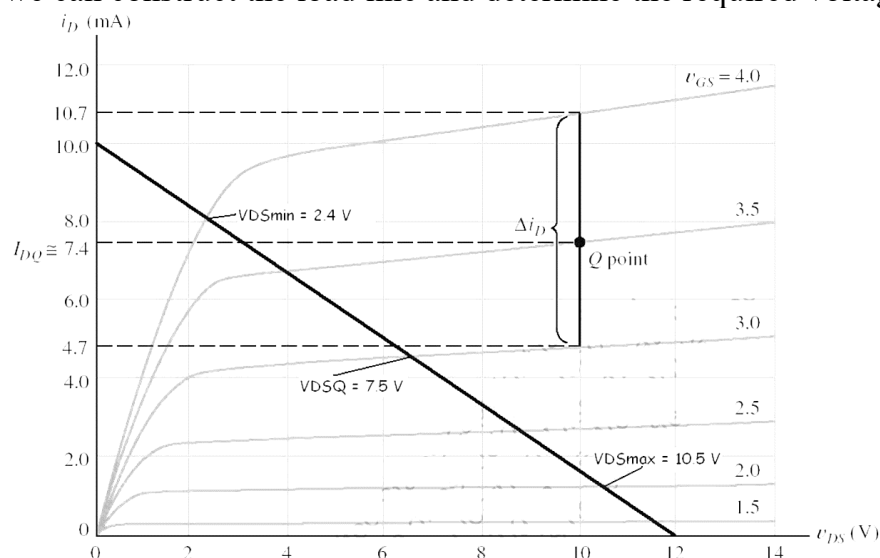**Solution:**


The Thevenin equivalent for the drain circuit contains a 12V source in series with a 1.2k $\Omega$  resistance. Then, we can construct the load line and determine the required voltages as shown:



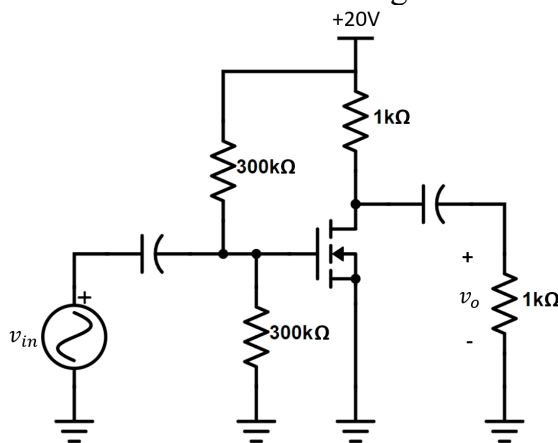**Q3. Problem 11.50**

Consider the common-source amplifier shown in the figure below. The NMOS transistor has  $KP = 50\mu A/V^2$ ,  $L = 5\mu m$ ,  $W = 500\mu m$ ,  $V_{to} = 1V$ , and  $r_d = \infty$ .

- Determine the values of  $I_{DQ}$ ,  $V_{DSQ}$ , and  $g_m$ .
- Compute the voltage gain, input resistance, and the output resistance, assuming that the coupling capacitors are short circuits for the ac signal.




**Solution:**

$$\begin{aligned}
 \text{a. } V_G &= V_{DD} \left( \frac{R_2}{R_1 + R_2} \right) = 20 \left( \frac{0.3}{1.7 + 0.3} \right) = 3V \\
 V_{GSQ} &= V_G = 3V \\
 K &= \frac{1}{2} KP \left( \frac{W}{L} \right) = 2.5 mA/V^2 \\
 I_{DQ} &= K(V_{GSQ} - V_{to})^2 = 10mA \\
 V_{DSQ} &= V_{DD} - R_D I_{DSQ} = 10V \\
 g_m &= 2\sqrt{KI_{DQ}} = 0.01S
 \end{aligned}$$

$$\begin{aligned} \text{b. } R'_L &= \frac{1}{\frac{1}{R_D} + \frac{1}{R_L}} = 500\Omega \\ A_V &= -g_m R'_L = -5 \\ R_{in} &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = 255k\Omega \\ R_o &= R_D = 1k\Omega \end{aligned}$$

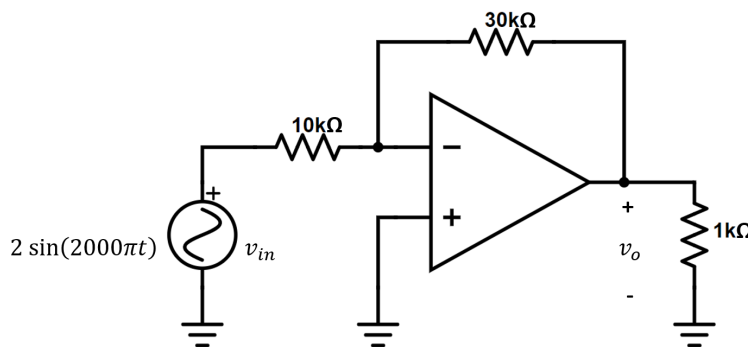
#### Q4. Problem 13.9

Consider the circuit shown in the figure below. Sketch  $v_{in}(t)$  and  $v_o(t)$  to scale versus time. The op amp is ideal.



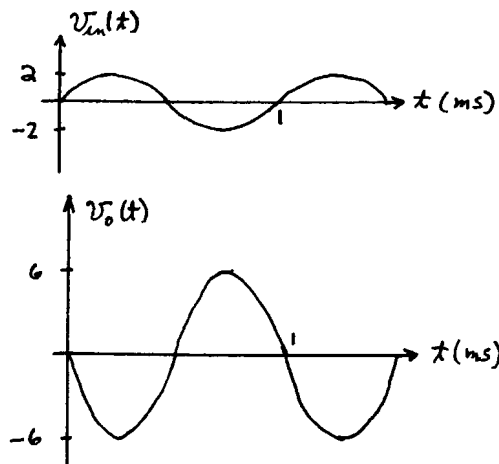
#### Solution:

This is an inverting amplifier having a voltage gain given by  $A_V = -\frac{R_2}{R_1} = -3$ . Thus, we have  $v_o(t) = -3 \times [2 \cos(2000\pi t)]$ . Sketches of  $v_{in}(t)$  and  $v_o(t)$  are:


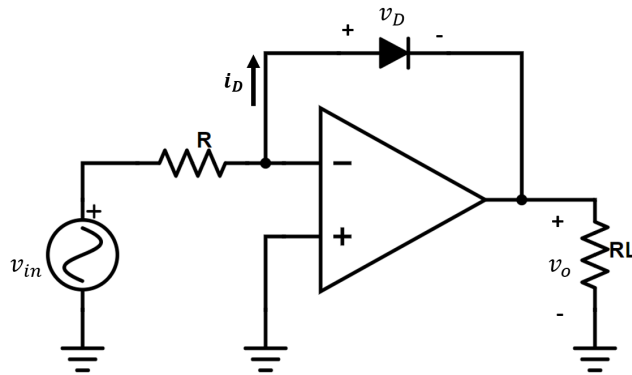
#### Q5. Problem 13.12

Consider the inverting amplifier shown in the figure below, in which one of the resistors has been replaced with a diode. Assume an ideal op amp,  $v_{in}$  positive, and a diode current given by  $i_D = I_s \exp(v_D/nV_T)$ . Derive an expression for  $v_o$  in terms of  $v_{in}$ ,  $R$ ,  $I_s$ ,  $n$ , and  $V_T$ .



**Solution:**

Using the summing-point constraint, we have

$$i_D = \frac{v_{in}}{R} = I_S \exp\left(\frac{v_D}{nV_T}\right)$$


$$v_o = -v_D$$

Solving, we have


$$v_o = -nV_T \ln\left(\frac{v_{in}}{RI_S}\right)$$

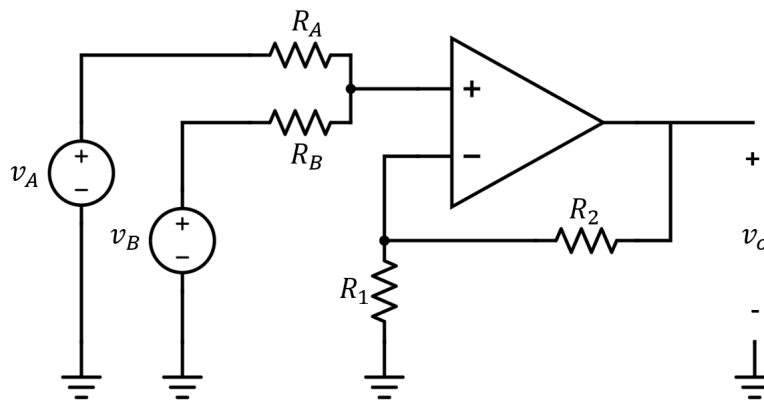**Q6. Problem 13.21**

Analyze the ideal-op-amp circuit shown in the figure below to find an expression for  $v_o$  in terms of  $v_A$ ,  $v_B$ , and the resistance values.



**Solution:**

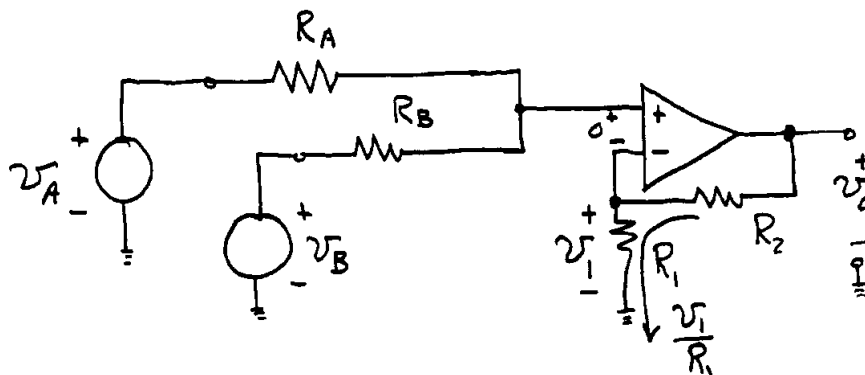

Writing a current equation at the noninverting input, we have

$$\frac{v_1 - v_A}{R_A} + \frac{v_1 - v_B}{R_B} = 0$$

Using the voltage-division principle we can write


$$v_1 = \frac{R_1}{R_1 + R_2} v_o$$

Using the second equation to substitute for  $v_1$  in the first equation and rearranging, we get:

$$v_o = \frac{R_1 + R_2}{R_1} \left( \frac{v_A R_B + v_B R_A}{R_A + R_B} \right)$$
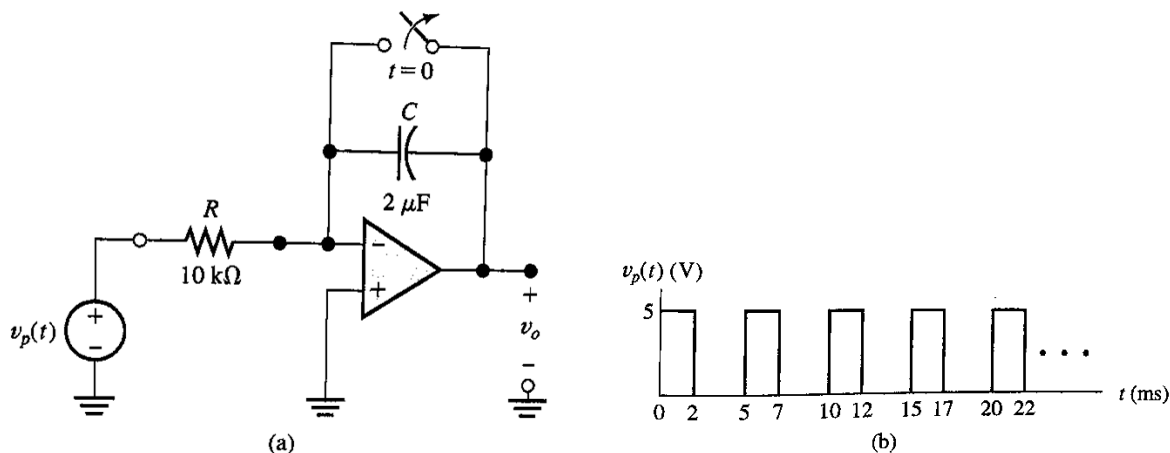
### Q7. Problem 13.74

Sketch the output voltage of the idea-op-amp circuit shown in the figure below to scale versus time. The circuit is shown in (a) and the input voltage  $v_p(t)$  is shown in (b).



### Solution:

This is an integrator circuit and the output is given by:

$$v_o(t) = -\frac{1}{RC} \int_0^t v_{in} dt = -50 \int_0^t v_{in} dt$$

A sketch of  $v_o(t)$  versus  $t$  is:

